

# MODELING AND DESIGN OF ULTRA-LOW-VOLTAGE CMOS CIRCUITS

Carlos Galup-Montoro and Márcio Cherem Schneider

**Integrated Circuits Laboratory**  
**Federal University of Santa Catarina, Florianópolis, Brazil**  
<http://www.lci.ufsc.br/>

**10th IEEE Latin American Symposium on Circuits  
Armenia – Colombia**



February 26, 2019

# Outline

- 1. Introduction**
- 2. All-region MOSFET model**
- 3. Low-voltage CMOS digital circuits**
- 4. Self-biased current source**
- 5. Ultra-low-voltage (ULV) oscillators**
- 6. ULV rectifiers & voltage multipliers**

# Motivations for low voltage

## 1. Scaling

 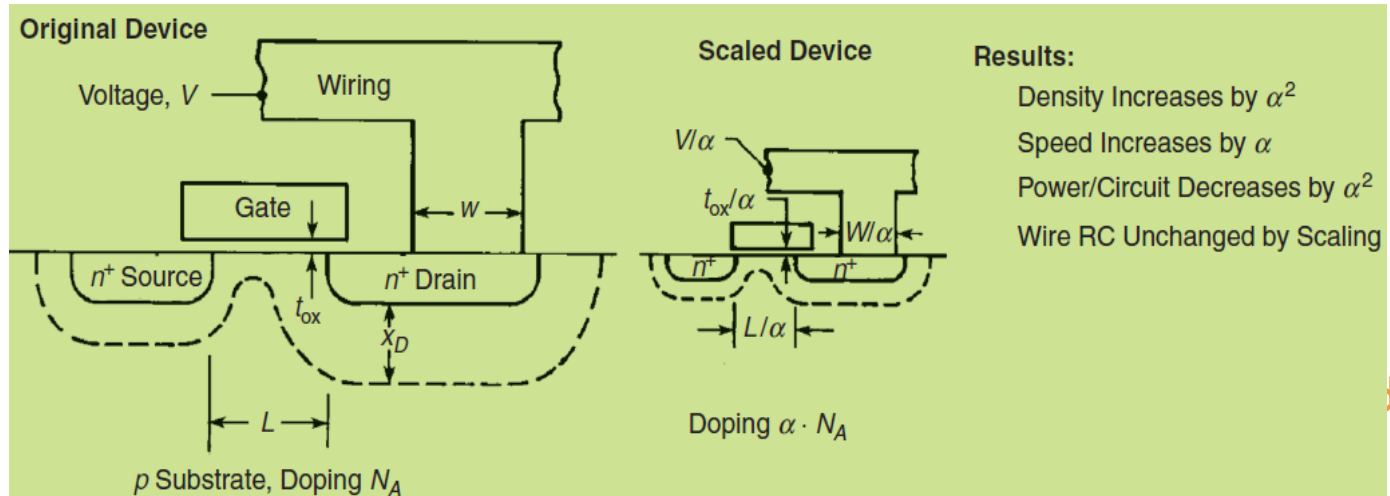

R. H. Dennard et al.  
IEDM 72 & IEEE JSSC,  
Oct. 1974


# Motivations for low voltage

## 2. Power dissipation


### Switching power

 **Power = Energy/transition \* f =  $C_L * V_{dd}^2$**

**Short-circuit power :**  
due to non-zero rise/fall times



**Leakage power  $\propto V_{DD}$**

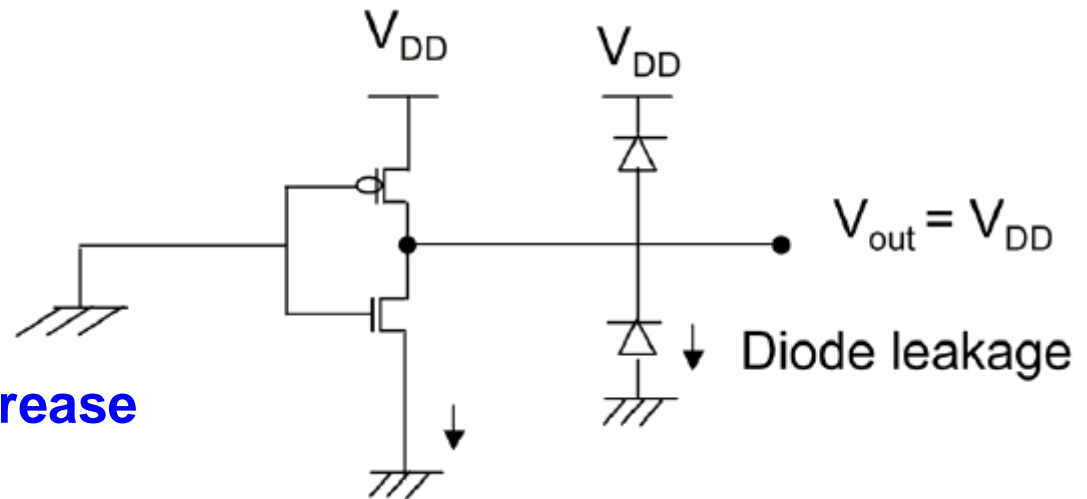


**Most effective way to decrease power is to lower  $V_{DD}$**

# Motivations for low voltage


## 3. Low supply voltages
 
### Thermoelectric generator

$$V_{o(\text{body-environment})} \approx 30 - 50 \text{ mV}$$




### Photovoltaic cell

 

$$V_{o(\text{dark room})} \approx 100 - 200 \text{ mV}$$

### Energy provided by trees


$$V_o \approx 20-200 \text{ mV}$$

 

\* Love et al, "Source of sustained voltage difference between the xylem of a potted ficus benjamina tree and its soil", 2008.

# The trend toward low supply voltages


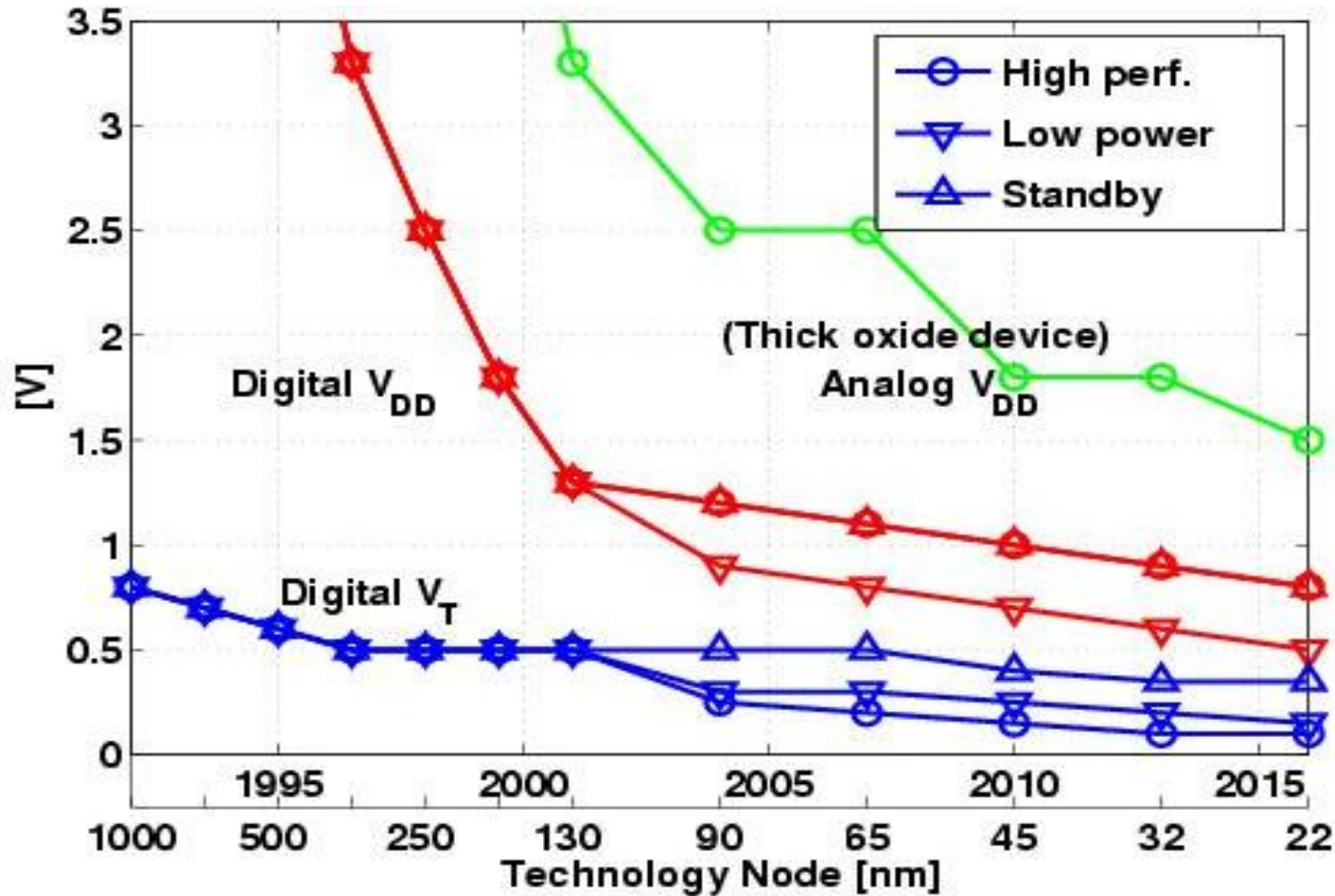
- Q1-Is there a lower bound for the supply voltage?
- Q2-What are the best technologies for ULV circuits?



Voltage scaling is slowing / stopping

<http://www.cisl.columbia.edu/grads/tuku/research/>
  
# BJTs vs. MOSFETs: structural differences



**BJT transconductance**

$$g_m = \frac{\partial I_C}{\partial V_B}$$

**Gate and source transconductances defined as**

$$g_m = \frac{\partial I_D}{\partial V_G} \quad g_{ms} = -\frac{\partial I_D}{\partial V_S}$$

The body effect reduces the gate transconductance with respect to the source transconductance

$$g_m = \frac{g_{ms}}{n}$$

$n$  ranges from  $\sim 1.1$  to  $1.5$  in bulk technologies

# Outline

1. Introduction
2. All-region MOSFET model
3. Low-voltage CMOS digital circuits
4. Self-biased current source
5. Ultra-low-voltage (ULV) oscillators
6. ULV rectifiers & voltage multipliers



# Weak and strong inversion models of the MOSFET

## Weak inversion (WI) & saturation

$$I_{WI} = I_0 e^{V_G/n\phi_t} \quad \rightarrow \quad I_{WI} = n g_m \phi_t$$

## Strong inversion (SI) ) & saturation

$$I_{SI} = \frac{1}{2n} \left( \mu C'_{ox} \frac{W}{L} \right) (V_G - V_{T0})^2 \quad \rightarrow \quad I_{SI} = \frac{n g_m^2}{2 \mu C'_{ox} (W/L)}$$

$V_{T0}$  is the threshold voltage at  $V_{SB} = 0$

$W/L$  is the aspect ratio,  $\mu$  is the mobility and  $C'_{ox}$  is the oxide capacitance per unit area

# All-region “interpolation” MOSFET model

$$I_{SI} = \frac{ng_m^2}{2\mu C'_{ox} (W/L)}$$

for  $g_m \rightarrow 0$   $I_{SI}$  is negligible

$$I_{WI} = ng_m \phi_t$$


while for  $g_m \rightarrow \infty$   $I_{WI}$  is negligible.

$$I_D = I_{WI} + I_{SI} = ng_m \phi_t \left[ 1 + \frac{g_m}{2\mu C'_{ox} \phi_t (W/L)} \right]$$

$$I_D = I_{WI} \left[ 1 + \frac{(W/L)_{th}}{(W/L)} \right]$$

$$g_m = (W/L)_{th} \mu (2C'_{ox} \phi_t)$$
 
# Aspect ratio vs. current excess in MOSFET design



$$I_D = I_{WI} \left[ 1 + \frac{(W/L)_{th}}{(W/L)} \right]$$

$$(W/L)_{th} = \frac{ng_m\phi_t}{4\mu nC'_{ox} \frac{\phi_t^2}{2}}$$

# $g_m/I_D$ model

$$I_D = ng_m\phi_t \left[ 1 + \frac{g_m}{2\mu C'_{ox}\phi_t(W/L)} \right] = ng_m\phi_t \left[ 1 + \frac{ng_m\phi_t}{4\mu nC'_{ox}\frac{\phi_t^2}{2}(W/L)} \right] \quad (I)$$

Defining the specific current  $I_S$  as  $I_S = I_{SH}(W/L); I_{SH} = \mu nC'_{ox}\frac{\phi_t^2}{2}$

$I_{SH}$  is the sheet specific current – technology parameter

the inversion level as  $i_f = \frac{I_D}{I_S}$   $i_f \gg 1$  strong inversion  
 $i_f \ll 1$  weak inversion

we rewrite (I) as

$$\frac{I_D}{ng_m\phi_t} = 1 + \frac{ng_m\phi_t i_f}{4I_D} \quad (II)$$

and, with painless algebra

$$\frac{ng_m\phi_t}{I_D} = \frac{2}{1 + \sqrt{1 + i_f}} \quad (III)$$

# The I-V MOSFET model (UICM)

Unified (I)current Control Model

$$\frac{g_m}{I_D} = \frac{2}{n\phi_t \left(1 + \sqrt{1+i_f}\right)} \quad g_m = \frac{g_{ms}}{n}$$

$$g_{ms} = -\frac{dI_D}{dV_S} = -I_S \frac{di_f}{dV_S} = \frac{2I_S}{\phi_t} \left(\sqrt{1+i_f} - 1\right) \Rightarrow -\frac{\phi_t}{2} \frac{di_f}{\sqrt{1+i_f} - 1} = dV_S \quad (I)$$

Integrating (I) between  $V_S$  and  $V_P$

$$V_P - V_S = \phi_t \left[ \sqrt{1+i_f} - \sqrt{1+i_p} + \ln\left(\sqrt{1+i_f} - 1\right) - \ln\left(\sqrt{1+i_p} - 1\right) \right]$$

$V_P$  is the pinch-off voltage

$i_p$  is the normalized pinch-off drain current



$$V_P \cong \frac{V_G - V_{T0}}{n}$$

Best choice  $i_p = 3!$

$$V_P - V_S = \phi_t \left[ \sqrt{1+i_f} - 2 + \ln\left(\sqrt{1+i_f} - 1\right) \right]$$
 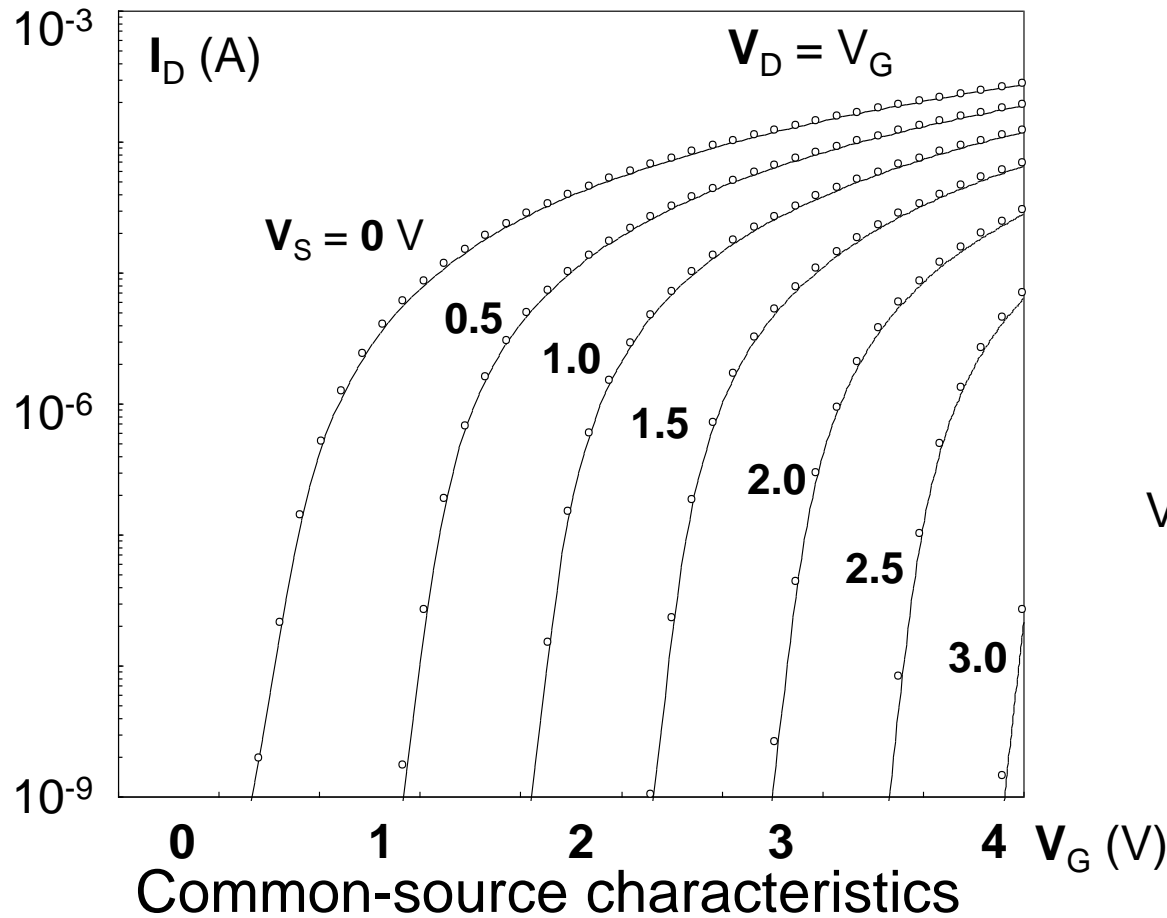
# The I-V relationship for a saturated MOSFET

$$V_P - V_S = \phi_t \left[ \sqrt{1 + i_f} - 2 + \ln(\sqrt{1 + i_f} - 1) \right]$$





For *ideal* MOSFET  $\rightarrow n=1 \rightarrow V_P - V_S = V_{GS} - V_{TO}$

# Forward and reverse currents

Symmetry of the rectangular-geometry MOSFET


$$I_D = I_F - I_R = I(V_G, V_S) - I(V_G, V_D)$$
 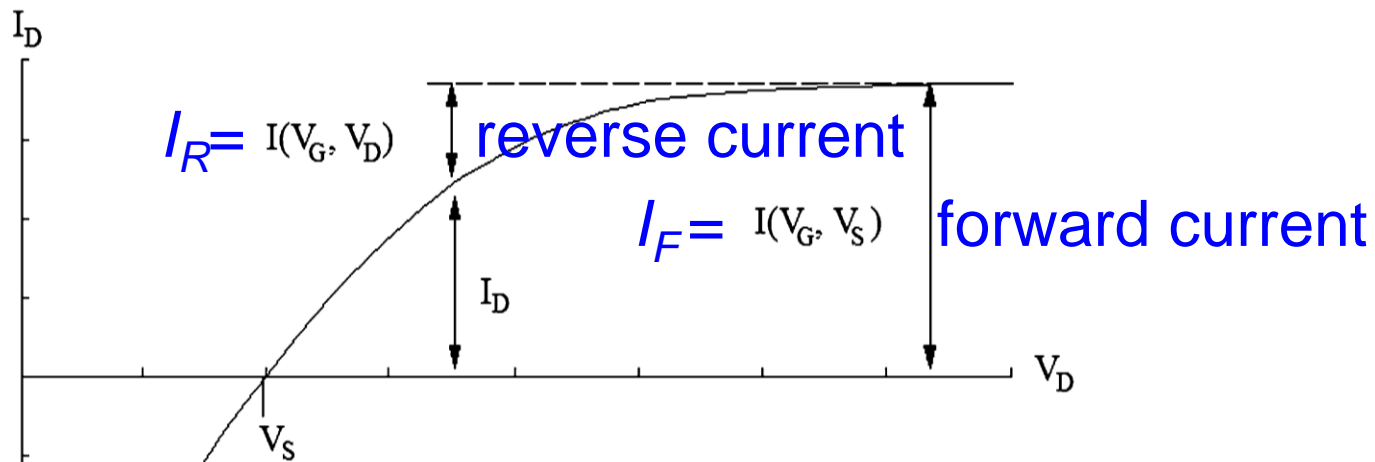
$$V_P - V_{S(D)} = \phi_t \left[ \sqrt{1 + i_{f(r)}} - 2 + \ln \left( \sqrt{1 + i_{f(r)}} - 1 \right) \right]$$


 
# Universal output characteristics

$$\frac{V_{DS}}{\phi_t} = \sqrt{1+i_f} - \sqrt{1+i_r} + \ln \left( \frac{\sqrt{1+i_f} - 1}{\sqrt{1+i_r} - 1} \right)$$



(a)  $i_f = 4.5 \times 10^{-2}$  ( $V_G = 0.7$  V); (b)  $i_f = 65$  ( $V_G = 1.2$  V); (c)  $i_f = 9.5 \times 10^2$  ( $V_G = 2.0$  V); (d)  $i_f = 3.1 \times 10^3$  ( $V_G = 2.8$  V); (e)  $i_f = 6.8 \times 10^3$  ( $V_G = 3.6$  V); (f)  $i_f = 1.2 \times 10^4$  ( $V_G = 4.4$  V).




# Transconductances

$$\Delta I_D = g_{mg} \Delta V_G - g_{ms} \Delta V_S + g_{md} \Delta V_D + g_{mb} \Delta V_B$$

$$g_{mg} (g_m) = \frac{\partial I_D}{\partial V_G}, g_{ms} = -\frac{\partial I_D}{\partial V_S}, g_{md} = \frac{\partial I_D}{\partial V_D}, g_{mb} = \frac{\partial I_D}{\partial V_B}$$

## Low-frequency small-signal model

 

$$g_{mg} = \frac{g_{ms} - g_{md}}{n}$$



$$g_{mg} \approx \frac{g_{ms}}{n}$$

**saturation**

# Outline

1. Introduction
2. All-region MOSFET model
3. Low-voltage CMOS digital circuits
4. Self-biased current source
5. Ultra-low-voltage (ULV) oscillators
6. ULV rectifiers & voltage multipliers

  
# THE CMOS INVERTER IN WEAK INVERSION - 1



**Note that:**

VDD	VoH ( Vi = 0 )	VoL ( Vi = VDD )
200 mV	200 mV	0mV
50 mV	<b>46.6 mV</b>	<b>3.4mV</b>
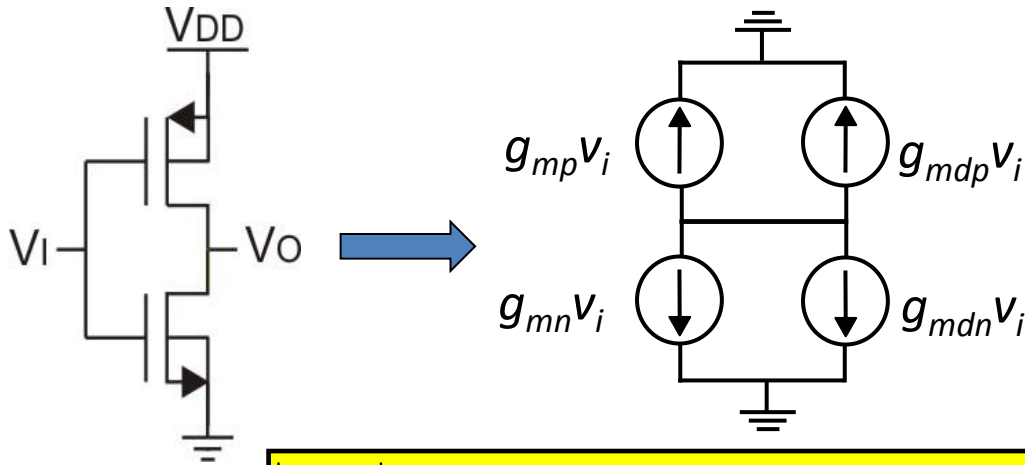
## THE CMOS INVERTER IN WEAK INVERSION - 2



In the ideal case of NMOS and PMOS transistors with the same strength, and  $V_i = V_o = V_{DD}/2$

$$g_{mdp} = g_{mdn} = g_{md}$$

$$g_{mp} = g_{mn} = g_m$$

$$\left. \frac{dV_o}{dV_i} \right|_{V_i=V_o=\frac{V_{DD}}{2}} = \frac{g_m}{g_{md}} = \frac{1}{n} \frac{g_{ms} - g_{md}}{g_{md}} = \frac{1}{n} \left( e^{V_{DS}/\phi_t} - 1 \right) = \frac{1}{n} \left( e^{V_{DD}/2\phi_t} - 1 \right)$$

**Regenerative logic** → Minimum operating supply voltage of the CMOS static logic gate must be such that the voltage gain is, at least, equal to unity, *i.e.*


$$\left. \frac{dV_o}{dV_i} \right|_{V_o=\frac{V_{DD}}{2}} = \frac{1}{n} \left( e^{V_{DD}/2\phi_t} - 1 \right) = 1$$

$$V_{DD\min} = 2\phi_t \ln(2)$$

$$V_{DD\min} = 36 \text{ mV at } 300 \text{ K}$$

**for  $n=1$**

# The classic CMOS Schmitt trigger

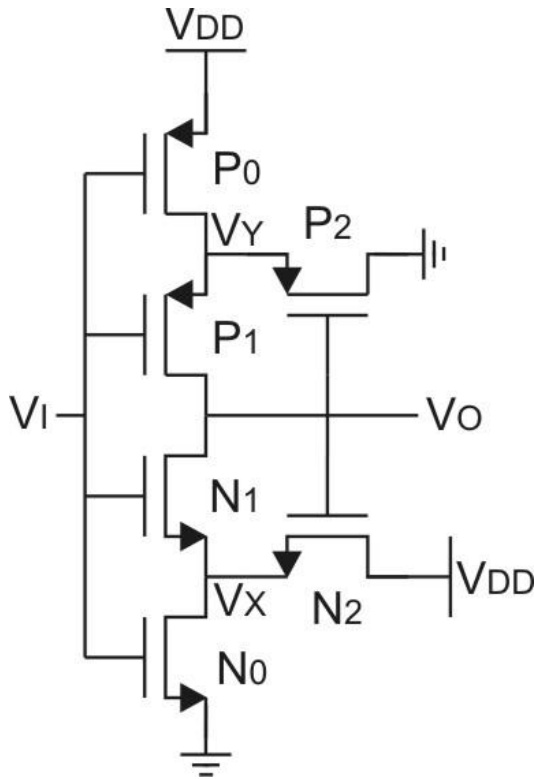

**6-transistor**



**Schmitt Trigger**

- *Positive feedback transistors (P2/N2) controlled by the output*
- *Modeled in strong inversion but not in weak inversion*
  - *For symmetric operation, corresponding NMOS and PMOS MOSFETs have the same current capability.*
- *Either gain improvement or hysteresis*
- *Logic from lower supply voltages*
- *Memory robustness ?*
- *Hysteresis dependent on V<sub>DD</sub> & relative transistor strength*



# The 6-T Schmitt trigger

Hysteresis mode

Amplifier mode

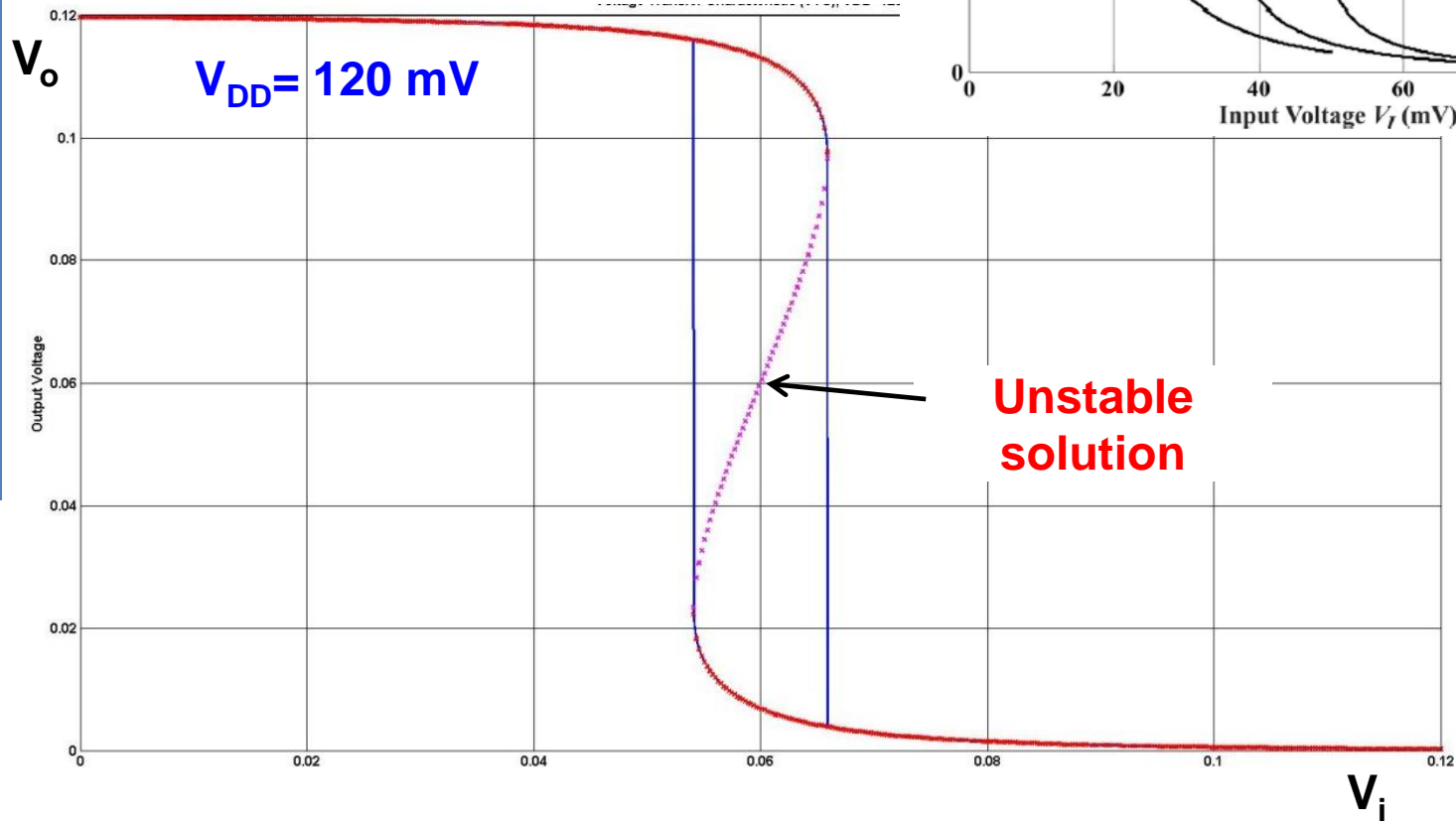 

# Schmitt Trigger small-signal model

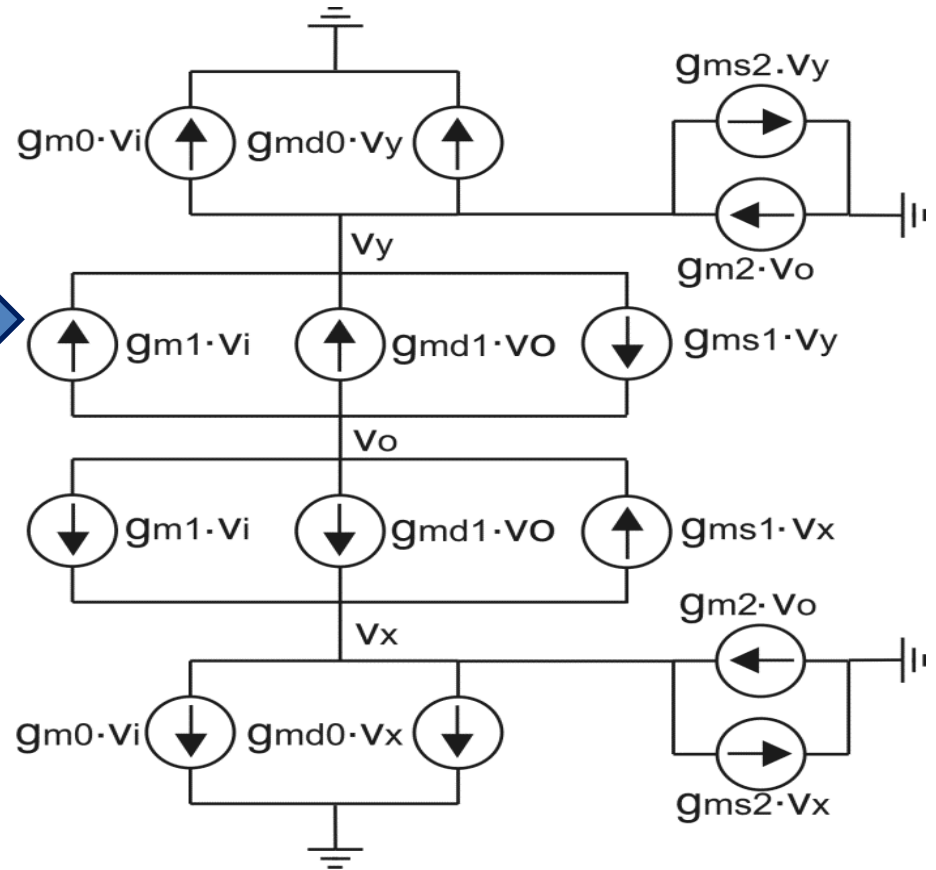 

$$A_{V,ST} = -\frac{g_{m1}}{g_{md1}} \frac{1 + \frac{g_{ms1}g_{m0}}{g_{m1}(g_{ms2} + g_{md0})}}{1 - \frac{g_{ms1}g_{m2}}{g_{md1}(g_{ms2} + g_{md0})}}$$

Voltage gain becomes  $\infty$  for


$$V_{DD} \approx 2\phi_t \ln \left( 2 + \frac{I_0}{I_2} + \frac{I_2}{I_0} + \frac{I_1}{I_2} \right)$$

Supply voltage at which hysteresis starts to appear


Theoretical minimum: ~75 mV, but practical minimum ~100 mV

# 6-T Schmitt trigger logic

*NOR gate*

 

*ST-NOR gate*

 




# Outline

1. Introduction
2. All-region MOSFET model
3. Low-voltage CMOS digital circuits
4. **Self-biased current source**
5. Ultra-low-voltage (ULV) oscillators
6. ULV rectifiers & voltage multipliers

# SELF-CASCADE MOSFET (SCM)

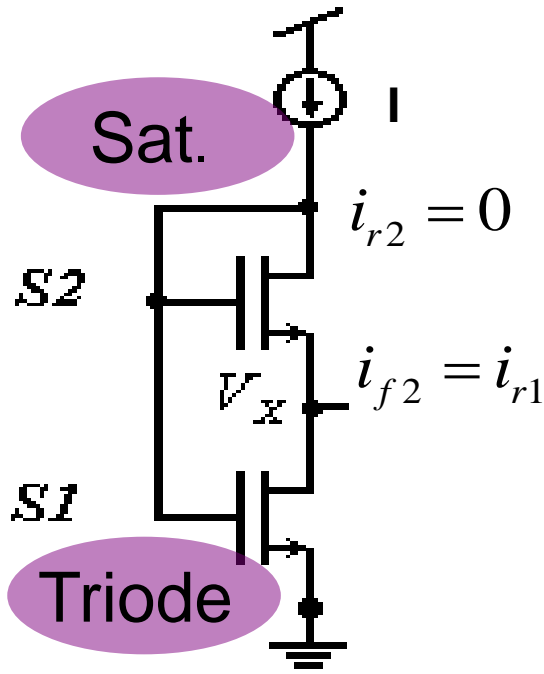

$$I = I_{S2} i_{f2} = I_{S1} (i_{f1} - i_{f2})$$



$$i_{f1} = \left(1 + \frac{I_{S2}}{I_{S1}}\right) i_{f2} = \left(1 + \frac{S_2}{S_1}\right) i_{f2} = \alpha i_{f2}$$




Applying UICM to M1

$$\frac{V_x}{\phi_t} = \sqrt{1 + i_{f1}} - \sqrt{1 + i_{f1}/\alpha} + \ln \left( \frac{\sqrt{1 + i_{f1}} - 1}{\sqrt{1 + i_{f1}/\alpha} - 1} \right)$$

In weak inversion,  $i_{f1} \ll 1$


$$\frac{V_x}{\phi_t} \rightarrow \ln \alpha$$

# SELF-CASCADE MOSFETs (SCM)

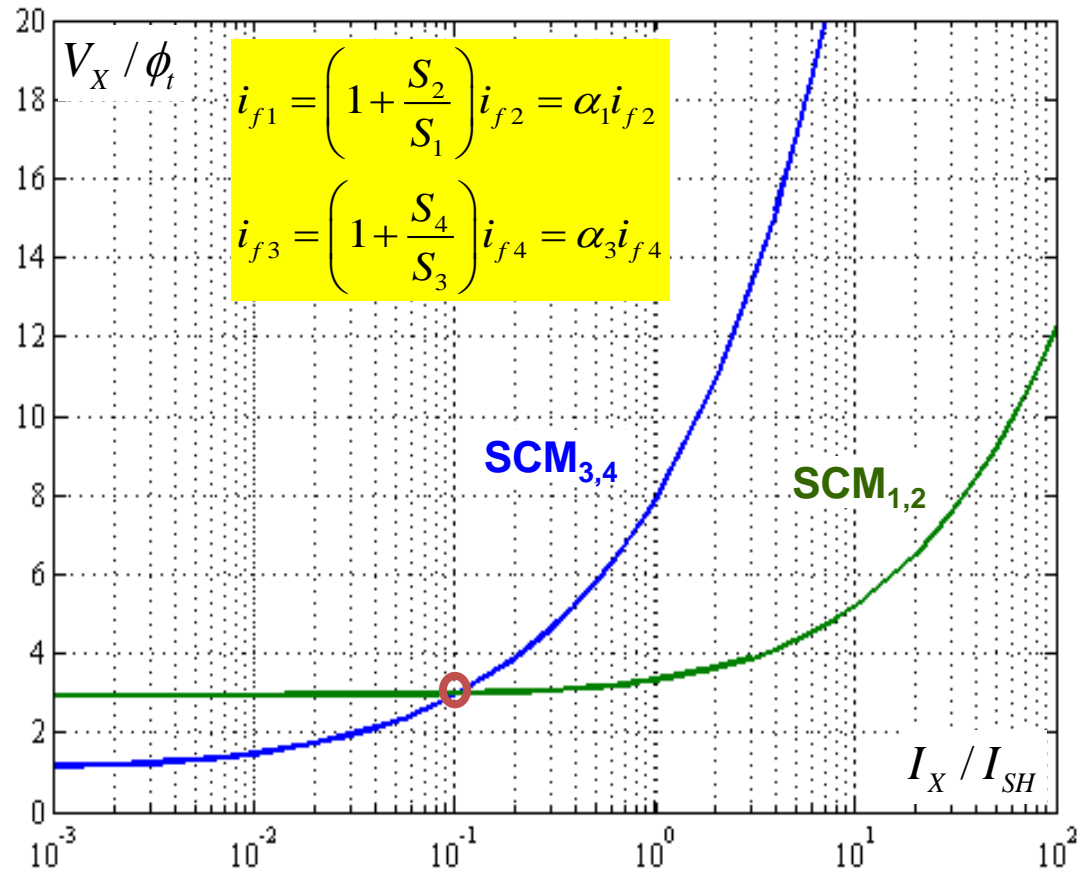  

**Hypothesis: both  $S_2$  &  $S_4$  in saturation**

# Self biased current source (SBCS)

 

If  $V_{\text{off}} = 0$  and  $M_1$  and  $M_2$  operate in WI  
it follows that

$$\ln \alpha_1 = \sqrt{1+i_{f3}} - \sqrt{1+i_{f3}/\alpha_3} + \ln \left( \frac{\sqrt{1+i_{f3}} - 1}{\sqrt{1+i_{f3}/\alpha_3} - 1} \right)$$

$$\alpha_1 = 1 + \frac{S_2}{S_1} \quad \alpha_3 = 1 + \frac{S_4}{S_3}$$


$$i_{f4} = \frac{i_{f3}}{\alpha_3}$$

•transistors are biased at constant inversion levels defined by aspect ratios, **independent of technology & temperature**

Coupling two SCMs via an op amp and a current mirror

# Using the SBCS for parameter extraction
 
## Threshold voltage ( $V_T$ ) and specific current ( $I_S$ ) extractor



$$\frac{V_G - V_{T0}}{n} - V_S = \phi_t \left[ \sqrt{1 + i_f} - 2 + \ln(\sqrt{1 + i_f} - 1) \right]$$

$$V_S = 0 \Rightarrow V_G = V_{T0} \text{ for } i_f = 3$$

$$i_{f3} = 3 \rightarrow V_{G3} = V_{T0}$$


reference current

$$I = I_{S4} i_{f4} = I_{S4} i_{f3} / (1 + S_4 / S_3)$$

$$I_S = I_{SH} (W / L); \quad I_{SH} = \mu n C'_{ox} \frac{\phi_t^2}{2}$$

- if mobility  $\sim T^{-1}$ , then  $I \sim I_{S4}$  is PTAT

# Inaccuracy of the SI approximation

 

Assuming M3 in SI in the linear region  
(equivalent to a resistor)

$$i_{f3} \approx \frac{\alpha_3 \ln^2 \alpha_1}{(\sqrt{\alpha_3} - 1)^2} \approx 4 \left( \frac{S_3}{S_4} \right)^2 \ln^2 \alpha_1$$


E. A. Vittoz, CCCD Workshop, Lund, 2003.

For  $\ln \alpha_1 = 4$  (practical maximum value)

$S_3/S_4$	$i_{f3}^1$	$i_{f3}^2$	$V_{GS} - V_{T0}$ ( $n = 1.2, V_{BS} = 0,$ $T = 300K$ )
10	6400	7200	2.57 V
2.5	400	610	0.65 V



<sup>1</sup> Strong inversion model. <sup>2</sup> Accurate all-region MOSFET model

# Variations of the SBCS topology

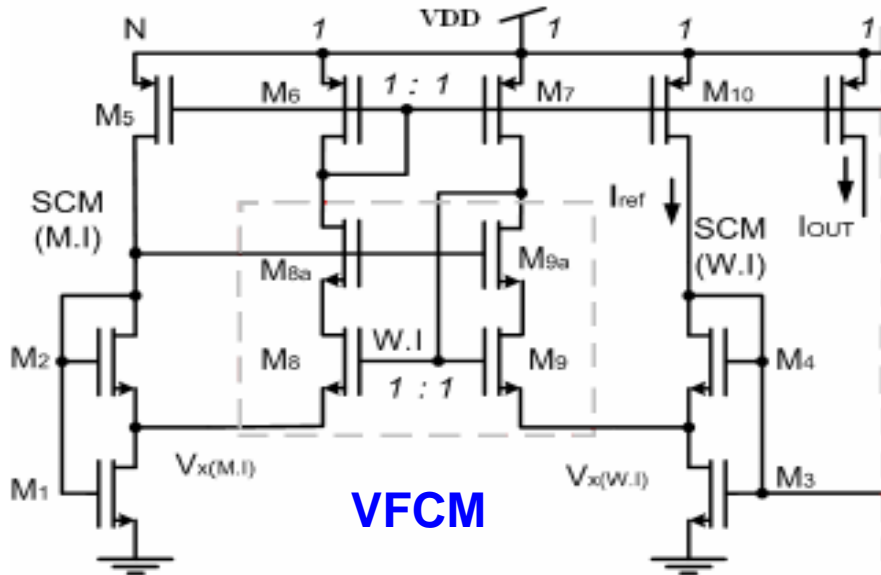

## Coupling two SCMs via a Voltage-Following Current Mirror

  E. M. Camacho-Galeano, C. Galup-Montoro and M. C. Schneider, "A 2-nW 1.1-V Self-Biased Current Reference in CMOS Technology", IEEE Trans. Circ. Syst. II, February 2005





H. J. Oguey and D. Aebischer, *IEEE J. Solid-State Circuits*, July 1997.

# Outline


1. Introduction
2. All-region MOSFET model
3. Low-voltage CMOS digital circuits
4. Self-biased current source
5. Ultra-low-voltage (ULV) oscillators
6. ULV rectifiers & voltage multipliers



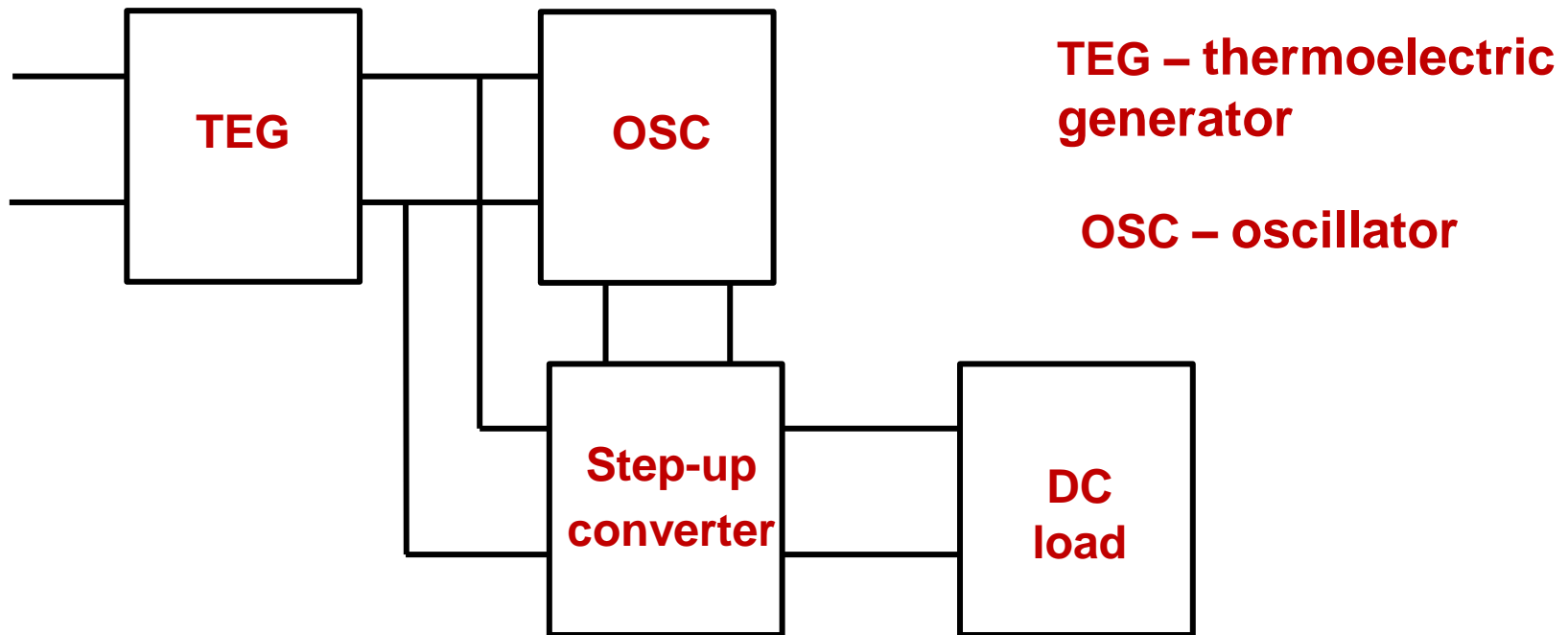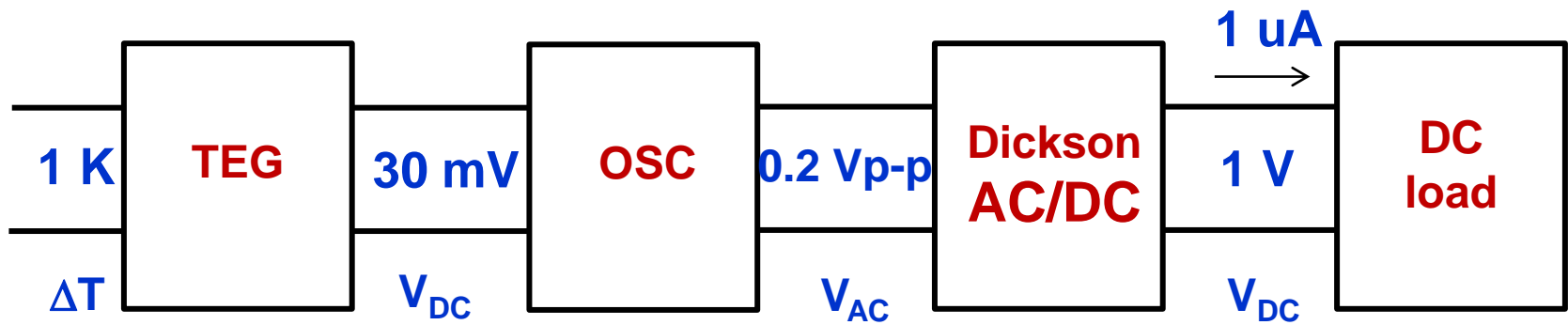
# Application of ULV oscillators in energy harvesters


 
# Inductive ring (X-coupled) oscillator - 1



Cross-coupled LC oscillator

 

$$\frac{V_{out}}{V_{in}} = - \frac{g_m}{g_{md} + G_P} \frac{1}{1 - j \tan \phi} = -1$$

$$\tan \phi = \frac{1 - LC\omega^2}{\omega L(g_{md} + G_P)}$$

Criterion for oscillation (Barkhausen)


$$\phi = 0 \text{ \& } V_{out}/V_{in} = -1$$

$$\frac{g_m}{g_{md} + G_P} = 1$$

$$\omega^2 LC = 1$$

What's the minimum  $V_{DD}$  for oscillation?

# Inductive ring oscillator - 2

 

Cross-coupled LC oscillator

Oscillation frequency  $\omega^2 LC = 1$

Voltage gain  $\frac{g_m}{g_{md} + G_P} = 1$

What's the minimum  $V_{DD}$  for oscillation?

Recall that  $g_m = \frac{g_{ms} - g_{md}}{n}$

Voltage gain=1  $\Rightarrow$

(i)  $\frac{g_{ms}}{g_{md}} = 1 + n \left( 1 + \frac{G_P}{g_{md}} \right)$


In weak inversion  $\Rightarrow$

(ii)  $\frac{g_{ms}}{g_{md}} = e^{V_{DS}/\phi_t} = e^{V_{DD}/\phi_t}$  since  $V_G = V_D = V_{DD}$

$$V_{DD,\min} = \phi_t \ln \left[ 1 + n \left( 1 + \frac{G_P}{g_{md}} \right) \right] = \phi_t \ln [1 + n] \quad \text{for } \frac{G_P}{g_{md}} \ll 1$$

Similar to the result (/2) of the CMOS inverter

# Inductive ring oscillator - 3

 


## Questions:

 
1. How to reduce  $V_{DD,min}$ ?
2. How to increase the  $V_{DD}$ -limited voltage swing?

Introduce voltage gain from drain to gate

Change topology, e. g., take advantage of CG gain





Enhanced swing IRO (ESRO)

 

Enhanced swing Colpitts oscillator (ESCO) \*

\* T. W. Brown et al, *IEEE JSSC*, Aug. 2011.
  
# The enhanced-swing Colpitts oscillator (ESCO)



$$G_{eq} = G_1 + \left(\frac{C_1}{C_1 + C_2}\right)^2 (G_2 + g'_m) \quad \frac{1}{L_{eq}} = \frac{1}{L_1} + \left(\frac{C_1}{C_1 + C_2}\right)^2 \frac{1}{L_2}$$

$$v_s \cong \frac{v_d}{1 + \frac{C_2}{C_1}} \rightarrow g_{ms} v_s - g_{md} v_d \cong g'_m v_s \quad g'_m = g_{ms} - \left(1 + \frac{C_2}{C_1}\right) g_{md}$$



For lossless inductors and capacitors

**Weak**  
  
**inversion**


$$V_{DDlim} = \frac{kT}{q} \ln \left( 1 + \frac{C_2}{C_1} \right)$$

# Colpitts oscillator: first prototype

## Off-the-shelf components



 
 


 24 // NMOS  
Zero-VT (ALD 1108)  
VT=59 mV, IS=11.2 uA





# Colpitts oscillator: second prototype


Zero-VT  
IBM 130 nm

  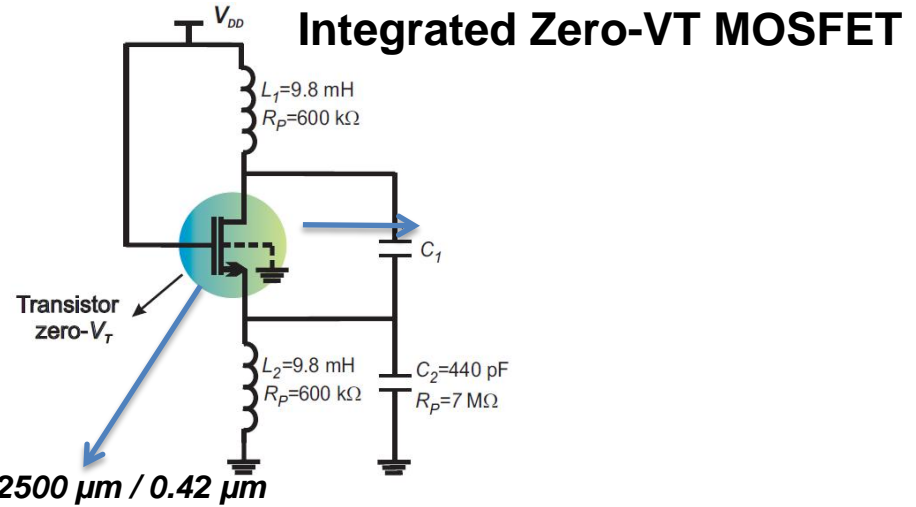 

# Colpitts oscillator – IC prototype

 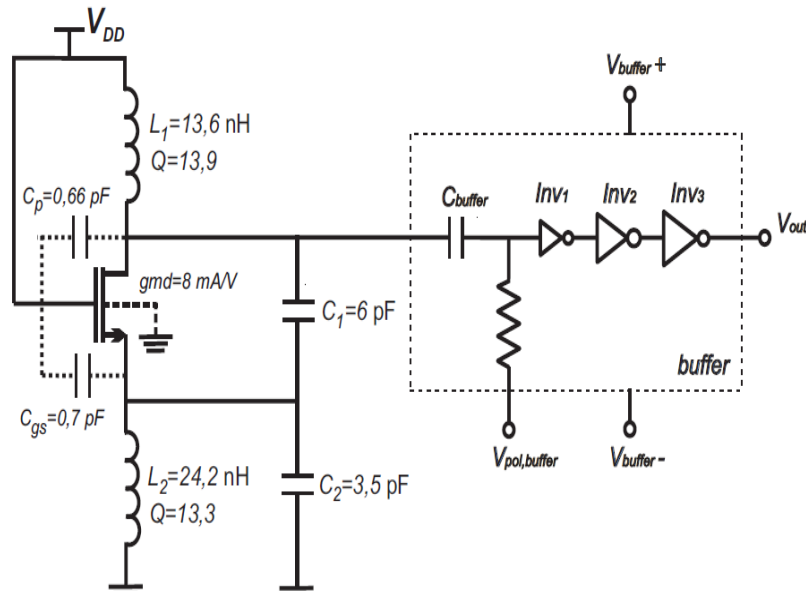

130 nm technology

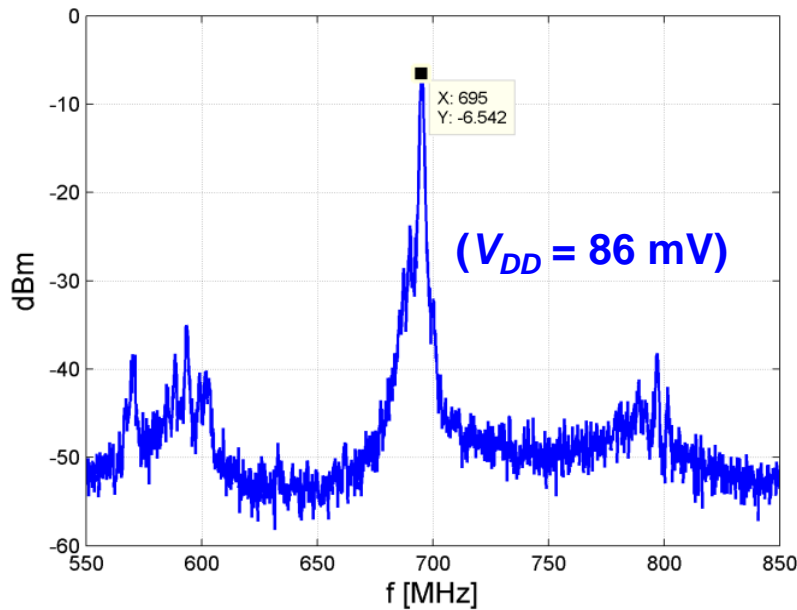



# Enhanced-swing ring oscillator (ESRO)


 
 
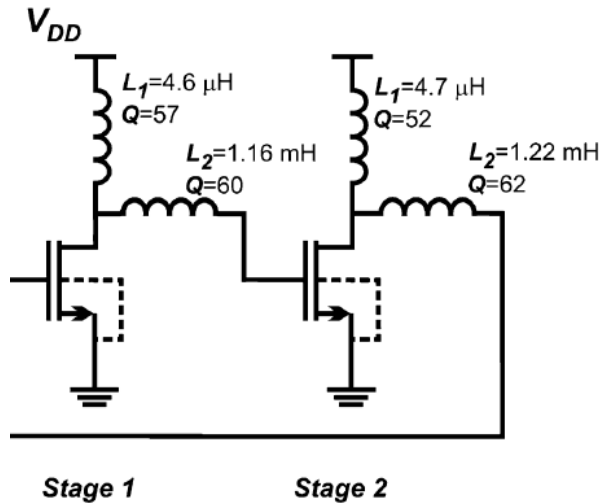


Fig. 12. Simulated (dotted line) and experimental (solid line) peak-to-peak gate voltage versus supply voltage of the ES inductive-load ring oscillator.

 


# Outline


1. Introduction
2. All-region MOSFET model
3. Low-voltage CMOS digital circuits
4. Self-biased current source
5. Ultra-low-voltage (ULV) oscillators
6. **ULV rectifiers & voltage multipliers**
 
# Ultra-low-voltage diode circuits

Dickson analysis of voltage multipliers: constant threshold voltage diode model, **not appropriate for low voltage operation**



$$V_L = V_P - V_{ON}$$

 


How to substitute the constant 'diode voltage drop' model?  
**Use the i-v characteristic of the diode and the load current**

$$I_D = I_S [e^{\frac{V_D}{n\phi_t}} - 1]$$

$$\phi_t = \frac{kT}{q}$$

$$n \sim 1 \text{ to } 1.5$$

# Single-stage voltage rectifier

 


- Steady state analysis
- Low ripple
- Square wave input

$$\frac{1}{T} \int_{-T/2}^{T/2} I_D dt = \frac{I_S}{T} \left[ \int_{-T/2}^0 \left( e^{\left( \frac{-V_P - V_o}{n\phi_t} \right)} - 1 \right) dt + \int_0^{T/2} \left( e^{\left( \frac{V_P - V_o}{n\phi_t} \right)} - 1 \right) dt \right] = I_L$$



$$\frac{V_o}{n\phi_t} = \ln \left[ \frac{\cosh(V_P / n\phi_t)}{1 + I_L / I_S} \right]$$

$$V_P > n\phi_t \Rightarrow V_o \cong V_P - \left( n\phi_t \ln \left( 2 \left( 1 + \frac{I_L}{I_S} \right) \right) \right) \longrightarrow \text{Diode "ON" voltage drop}$$

# Single-stage voltage rectifier

 

 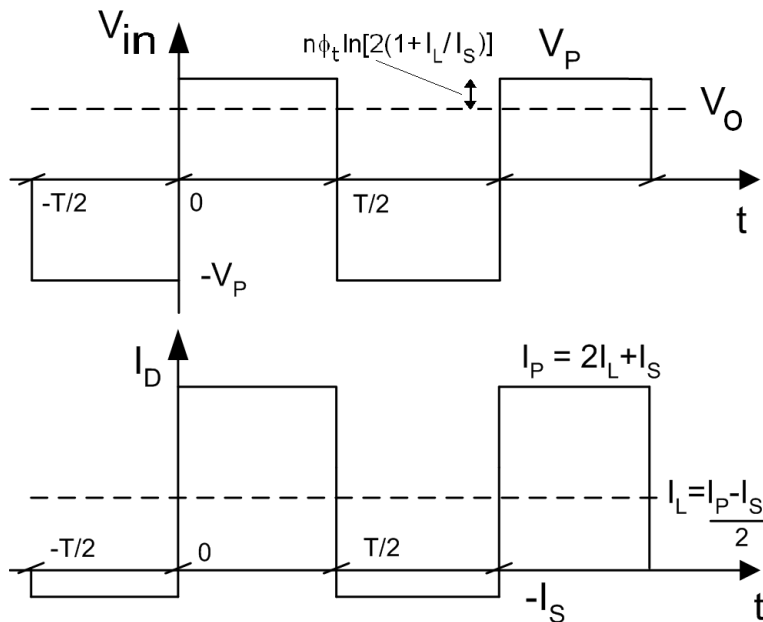
$$V_o \cong V_P - n\phi_t \ln \left( 2 \left( 1 + \frac{I_L}{I_S} \right) \right)$$



# The voltage multiplier

## N-stage voltage multiplier

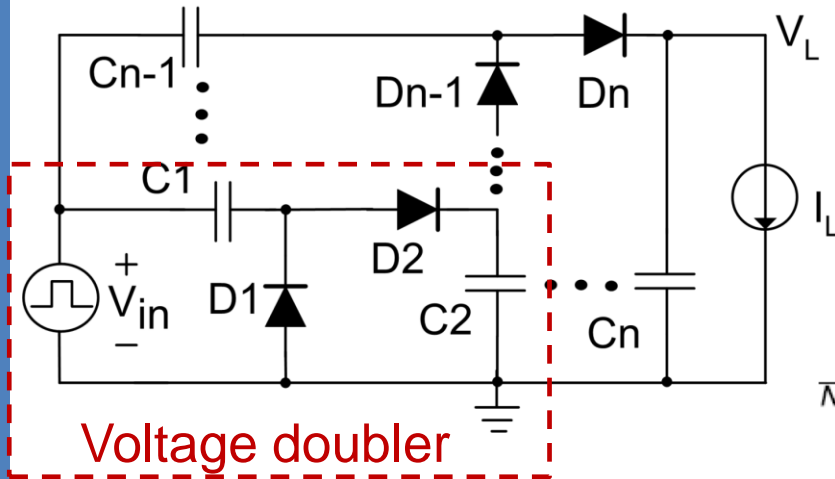

Output voltage

$$\frac{V_L}{n\phi_t} = N \ln \left[ \frac{I_0(V_A/n\phi_t)}{1 + I_L/I_S} \right]$$


Modified Bessel function, first kind, order zero

Power conversion efficiency (PCE)

$$PCE = \frac{P_{load}}{P_{in}}$$

PCE is maximized for

 
$$\frac{I_L}{I_S} = \frac{V_L}{Nn\phi_t}$$





# The voltage multiplier - 3
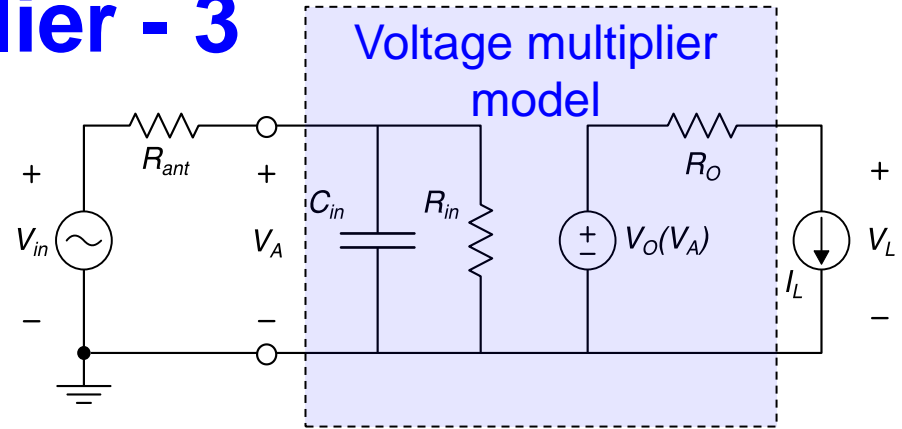
## Model of the N-stage voltage multiplier

$$k_c = \frac{R_{ant} V_L I_L}{(n\phi_t)^2}$$







  Design for minimum available power/maximum range in terms of  $k_c$



# AC/DC converter in 130 nm CMOS technology


## 24-stage rectifier

  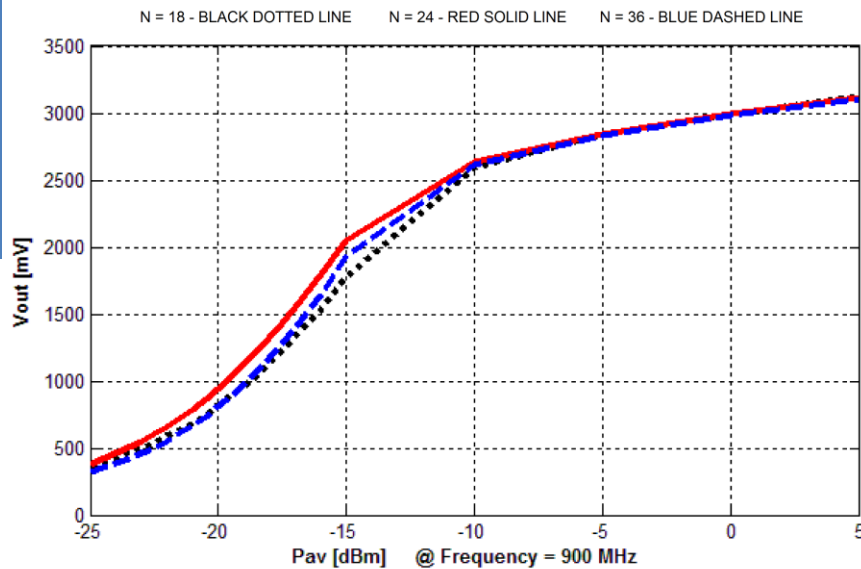 


**Matching network**



# What about diodes?



 


 - Low (zero)-VT
- Standard-VT
- pn junction





**Diode-connected zero-VT MOSFET**  
**- high drive capability ( $W/L \cong 7$ )**

# Zero-VT MOSFETs

  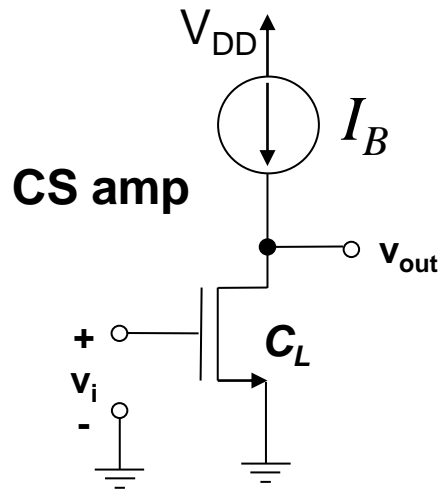

- $I_D \times V_{DS}$  ( $V_S = V_B$ ) characteristics for a zero-VT transistor with  $W/L = 2500\mu\text{m}/420\text{nm}$ . For  $V_{GS} = 0$  V and  $V_{DS} = 25$  mV the values of the common-gate and common-source gains are 1.56 and 0.53, respectively (moderate inversion operation).

# Energy harvester

 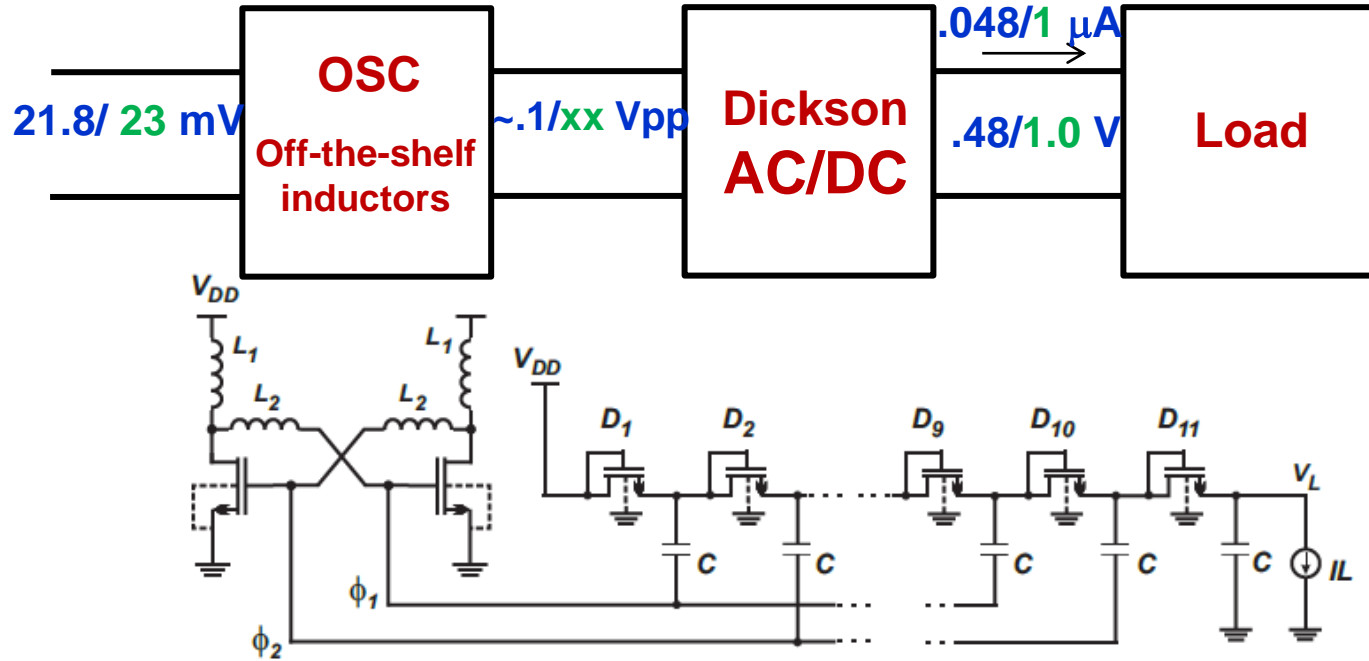

# References

- Márcio Cherem Schneider and Carlos Galup-Montoro, "[CMOS Analog Design Using All-Region MOSFET Modeling](#)", Cambridge University Press, 2010
- N. Lotze and Y. Manoli, "A 62mV 0.13um CMOS standard-cell-based design technique using Schmitt-Trigger logic", *IEEE Journal of Solid-State Circuits*, vol. 47, no. 1, pp 47-60, Jan 2012.
- A. J. Cardoso *et al.* , "Analysis of the rectifier circuit valid down to its low-voltage limit" , *IEEE Transactions on Circuits and Systems I: Regular Papers*, Jan. 2012.
- M. B. Machado *et al.* , "On the minimum supply voltage for MOSFET oscillators", *IEEE Transactions on Circuits and Systems I: Regular Papers*, Feb 2014.
- "[Ultra-low-voltage oscillators with application to energy harvesting circuits](#)", M. B. Machado, PhD, UFSC, August 2014, [http://www.lci.ufsc.br/work\\_doct.html](http://www.lci.ufsc.br/work_doct.html)
- R. H. Dennard, "Past Progress and Future Challenges in LSI Technology", *IEEE Solid-State-Circuits Magazine*, Spring 2015.
- L . G. de Carli *et al.* , "Maximizing the Power Conversion Efficiency of Ultra-Low-Voltage CMOS Multi-Stage Rectifiers," *IEEE Transactions on Circuits and Systems I: Regular Papers*, April 2015.
- L. A. P. Melek *et al.*, "Analysis and design of the classical CMOS Schmitt trigger in subthreshold operation", *IEEE Trans. Circuits and Systems-I: Reg. Papers*, April 2017.