

ULTRA-LOW-VOLTAGE IC DESIGN

Carlos Galup-Montoro and Márcio Cherem Schneider

Laboratório de Circuitos Integrados
Universidade Federal de Santa Catarina, Florianópolis, Brazil
<http://www.lci.ufsc.br/>

Outline



- **1 Introduction to ultra-low-voltage (ULV) CMOS**
- **2 Subthreshold MOSFET model**
- **3 Subthreshold CMOS logic and Schmitt trigger**
- **4 ULV rectifiers**
- **5 ULV oscillators**

Chapter 1

Introduction to ultra-low-voltage CMOS

Motivations for low voltage

1. Scaling

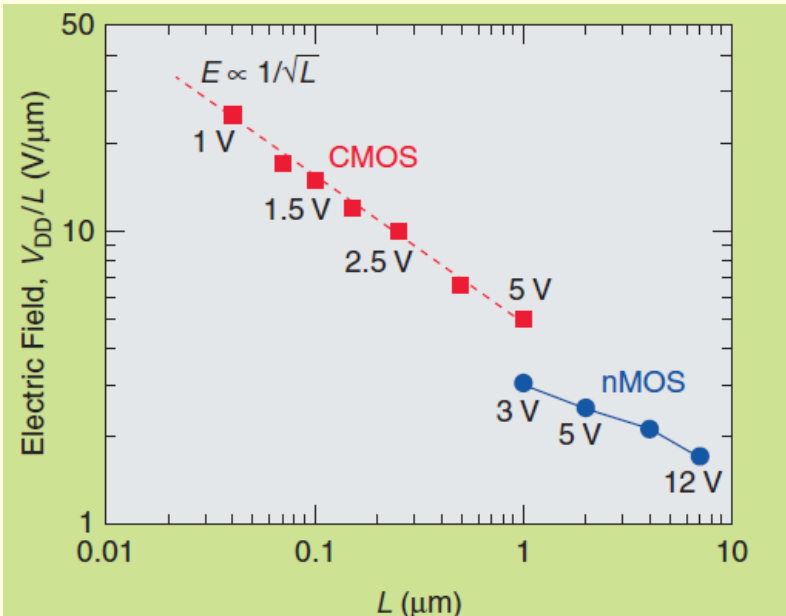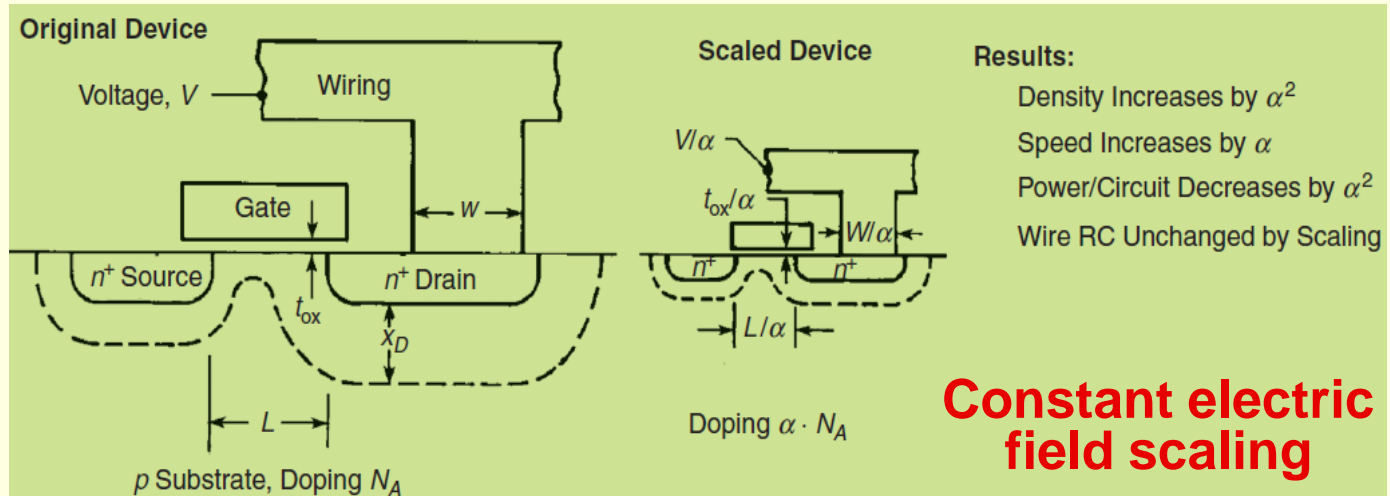

R. H. Dennard et al.
IEDM 72 & IEEE JSSC,
Oct. 1974


Motivations for low voltage

2. Power dissipation

Switching power


$$\text{Power} = \text{Energy/transition} * f = C_L * V_{dd}^2$$

 Short-circuit power :
due to non-zero rise/fall times



Leakage power $\propto V_{DD}$

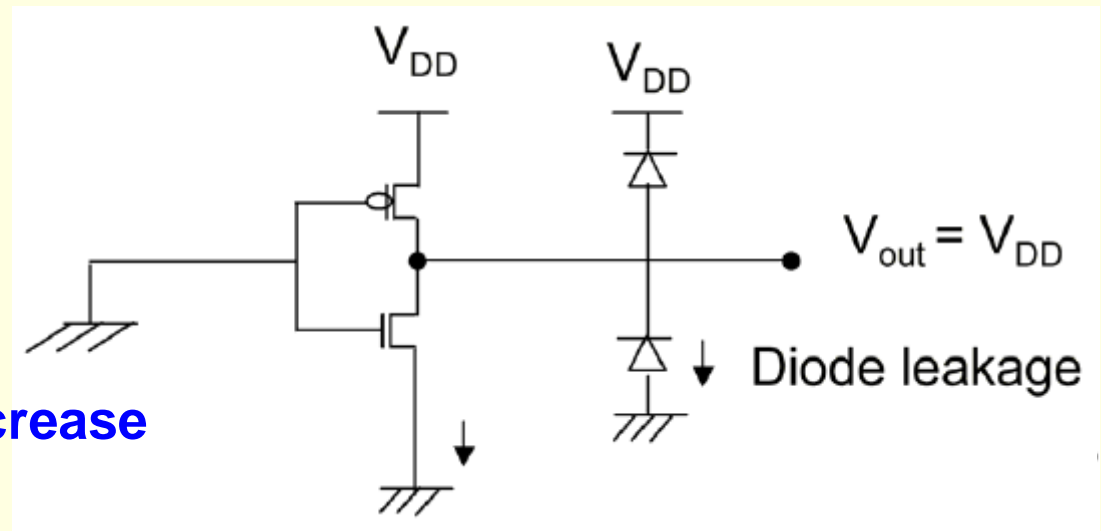Most effective way to decrease
power is to lower V_{DD}



Sub-threshold current


Motivations for low voltage

3. Low supply voltages


Thermoelectric generator

$$V_{o(\text{body-environment})} \approx$$

30 - 50 mV

 

Photovoltaic cell

 


$$V_{o(\text{dark room})} \approx$$

100 - 200 mV

Energy provided by trees

$$V_o \approx \mathbf{20-200\ mV}$$


pH difference

 

* Love et al, "Source of sustained voltage difference between the xylem of a potted ficus benjamina tree and its soil", 2008.

The trend toward low supply voltages

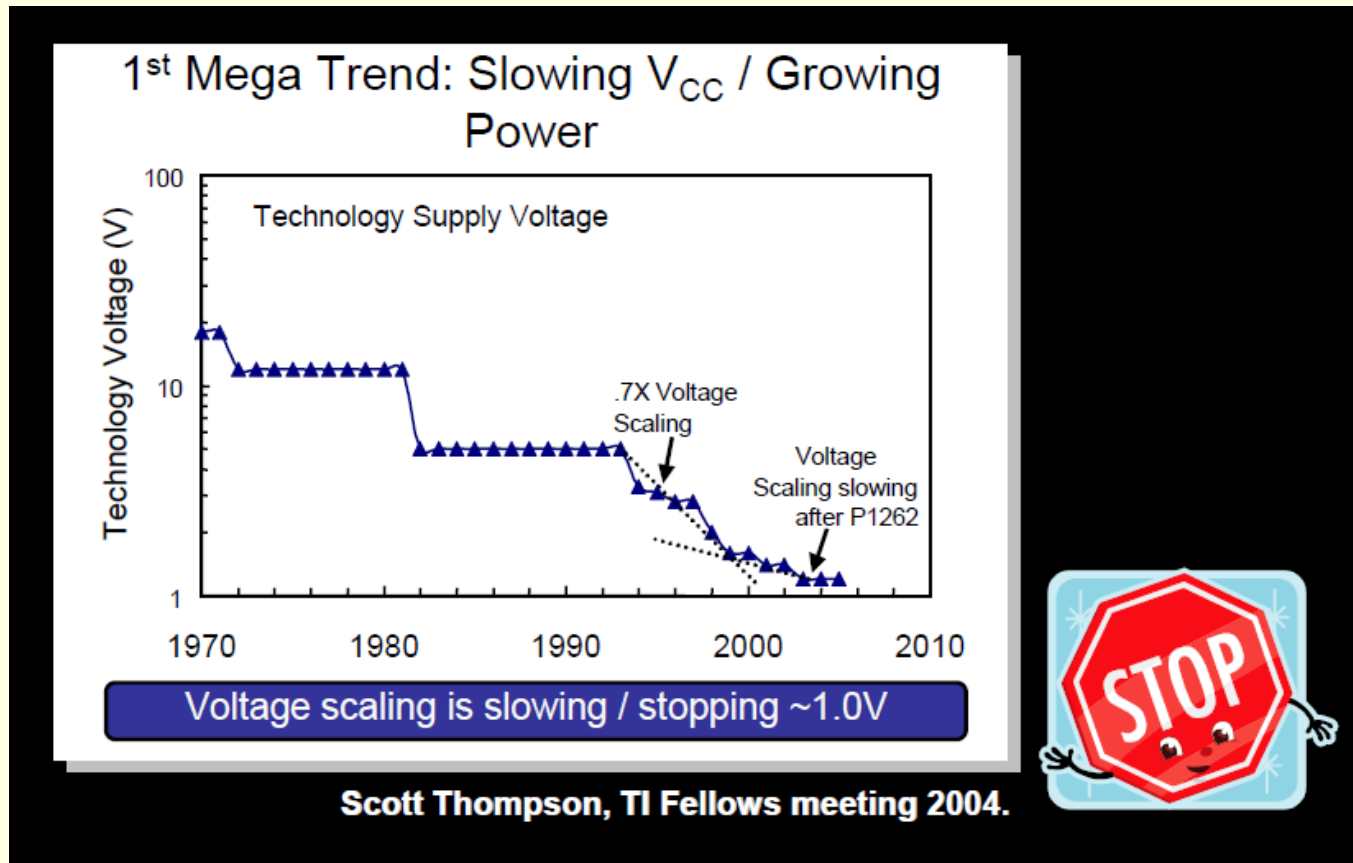
- Q1-Is there a lower bound for the supply voltage?
- Q2-What are the best technologies for ULV circuits?




Fundamental limits on supply voltage

From thermodynamics

 What is the minimum energy stored in a capacitor to ensure that the binary states are distinguishable in the presence of thermal noise?



 Any energy storage element (or “degree of freedom”) in thermal equilibrium holds an average noise energy of $kT/2$.




$$\overline{\frac{1}{2} C v_{no}^2} = \frac{kT}{2}$$

$$\overline{v_{no}^2} = \frac{kT}{C}$$

Fundamental limits on supply voltage

From thermodynamics

 What is the minimum energy stored in a capacitor to ensure that the binary states are distinguishable in the presence of thermal noise (Theis & Solomon 2010)?



The charge Q_{bit} stored in C is

$$Q_{bit} = CV_{bit} \Rightarrow V_{bit} > \frac{kT}{Q_{bit}} = \frac{kT}{Nq}$$

N is the number of electrons and $q=1.6 \times 10^{-19}$ C is the electron charge

The bit (=1) energy is $\frac{1}{2}CV_{bit}^2$

To distinguish bit energy from noise energy we must have

$$\frac{1}{2}CV_{bit}^2 > \frac{kT}{2} \Rightarrow V_{bit}^2 > \frac{kT}{C}$$

$$N = 1 \Rightarrow V_{bit} > \frac{kT}{q} = 25.9 \text{ mV}, C > 6.18 \text{ aF}$$

$$N = 1000 \Rightarrow V_{bit} > 25.9 \text{ } \mu\text{V}, C > 6.18 \text{ pF}$$

Eight standard deviations give an error probability of $\sim 10^{-15}$

$$V_{bit} > 8 \frac{kT}{Nq}$$

Thermal noise limits for supply voltages of logic and static memory

$$V_{no}^2 = kT/C \quad (I)$$

Output node capacitance


$$V_{out} = Nq/C \quad (II)$$

Number of electrons stored in the output node

For $V_{min} = V_{out} \sim V_{no}$

$$V_{min} = V_{out} = (1/N)kT/q$$

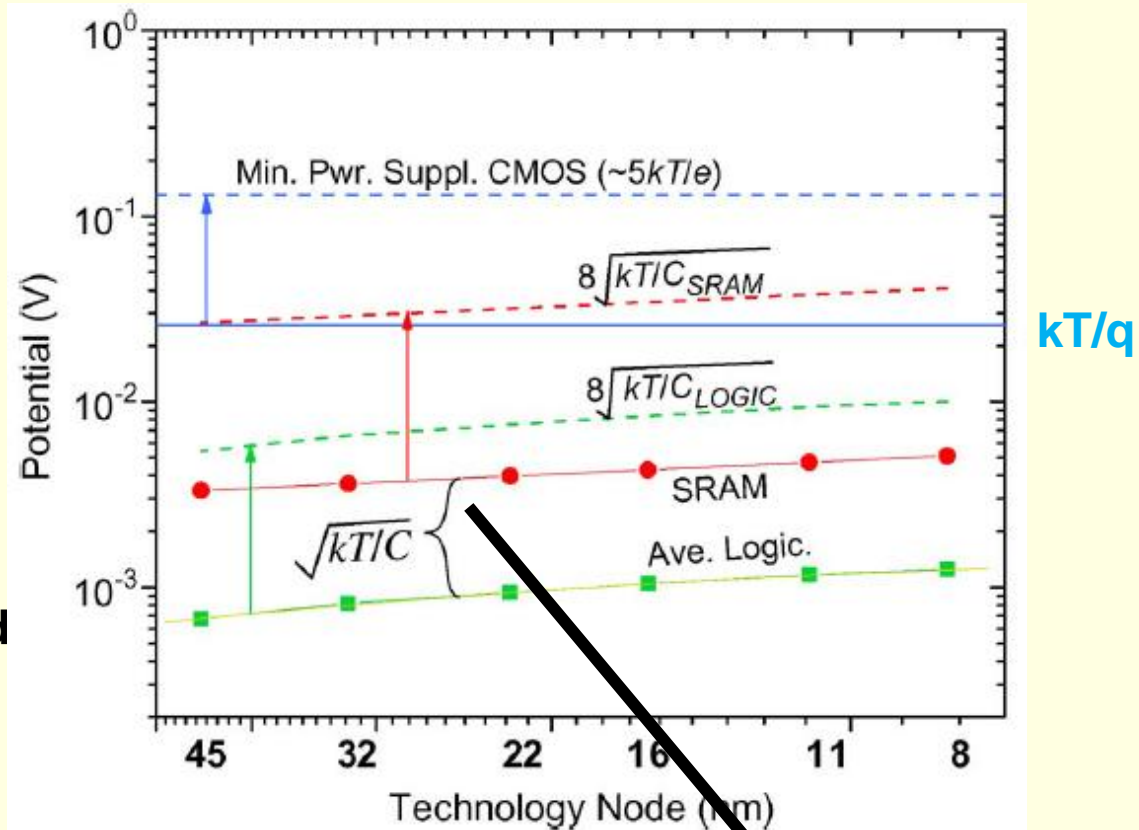
$N = 1$ circuit storing a single electron in its output node



There is large room and need for a millivolt switch

Fundamental limits on supply voltage

 From device physics - Minimum supply voltage for the standard CMOS inverter



**CMOS inverter transfer characteristics
(Swanson and Meindl, IEEE JSSC 1972)**


Regenerative logic requires that

$$| \text{Voltage gain} | \geq 1$$



Prof. James Meindl:
Theoretically, the minimum supply voltage for a CMOS inverter is $2 (\ln 2) (kT/q) = 36 \text{ mV}$ at room temperature (IEEE JSSC, 2000)

Searching for the millivolt switch

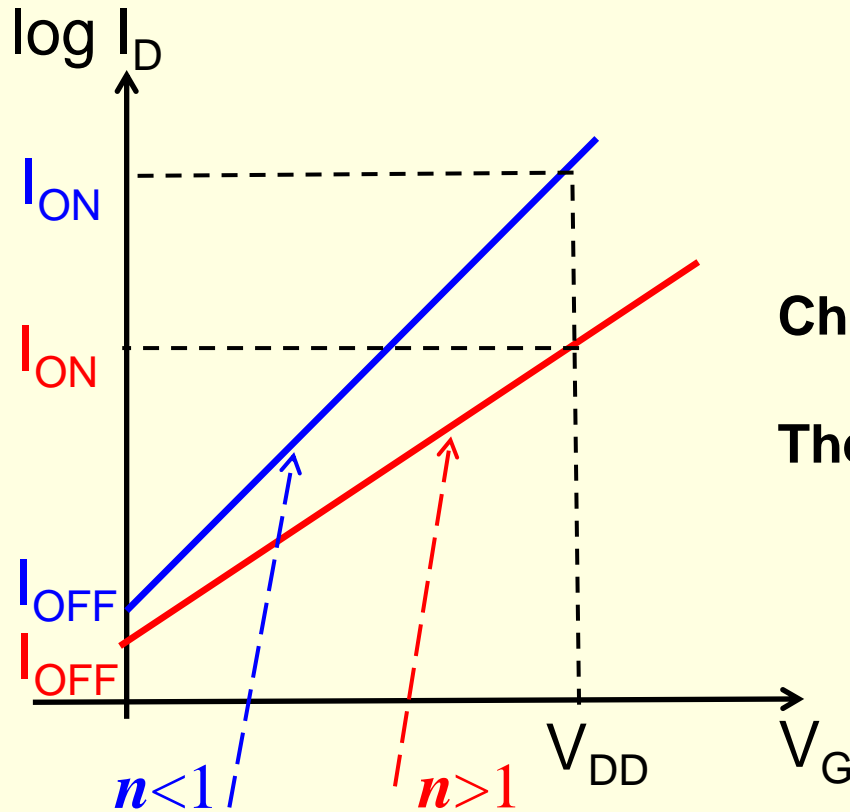

$$n < 1 \quad C_D < 0 \quad ???$$


Change of physical principle:

Thermal injection \rightarrow Tunneling

$$I_D \propto \exp(V_G / n\phi_t)$$

$$\text{MOSFET} \rightarrow n = 1 + \frac{C_D}{C_{ox}}$$

Searching for the millivolt switch

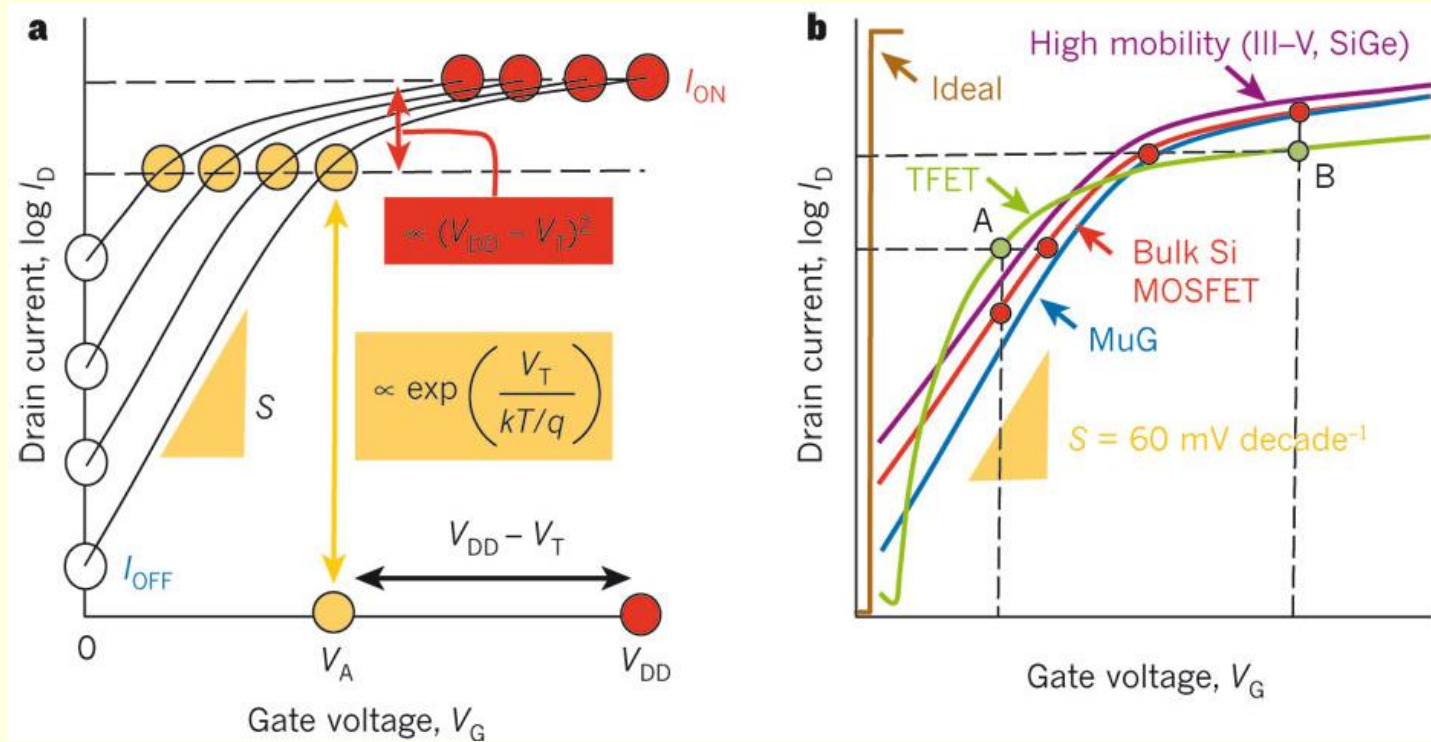


To outperform CMOS transistors, target parameters for Tunnel FETs are:


- $I_{ON} \sim$ hundreds of mA;
- $S_{avg} < 60 \text{ mV per decade}$ for five decades of current;
- $I_{ON}/I_{OFF} > 10^5$; and $V_{DD} < 0.5 \text{ V}$.

[Ionescu & Riel, Tunnel field-effect transistors as energy-efficient electronic switches, Nature 479, 329–337, 2011.](#)

Searching for the millivolt switch

 


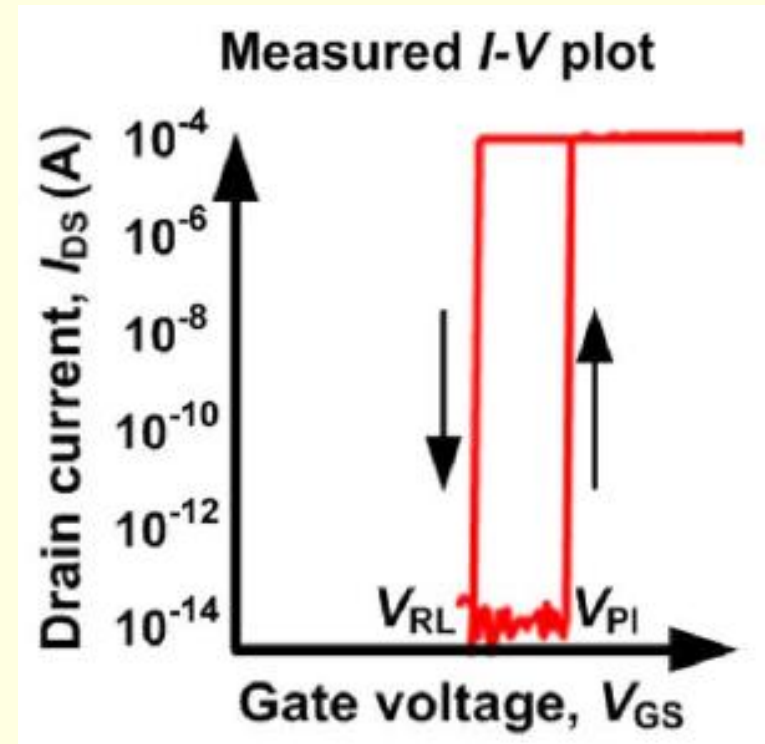(a) Mechanical switch. When $V_{GS} > V_{PI}$, the electrostatic force is sufficient to bring the source into contact with the drain.



(b) Current versus gate voltage characteristics for a mechanical switch. The switch exhibits a hysteretic switching behavior $V_{RL} \neq V_{PI}$

Ultra-low voltage (ULV) CMOS

 

References



- R. M. Swanson and J. D. Meindl, "Ion-implanted complementary MOS transistors in low voltage circuits," *IEEE J. Solid State Circuits*, Apr. 1972.
- T. N. Theis and P. Solomon, "In quest of 'the next switch': prospects for greatly reduced power dissipation in a successor to the silicon field-effect transistor," *Proceedings of the IEEE*, Dec. 2010.
- V. Pott *et al.* "Mechanical computing redux: relays for integrated circuit applications," *Proceedings of the IEEE*, Dec. 2010
- D. Perlmutter, Sustainability in silicon and systems development, *2012 IEEE International Solid-State Circuit Conference*, San Francisco, CA, Feb. 2012.
- R. H. Dennard, "Past Progress and Future Challenges in LSI Technology", *IEEE Solid-State-Circuits Magazine*, Spring 2015.
- Gordon E. Moore (INTEL), "No exponential is forever"
<http://ieeexplore.ieee.org/stamp/stamp.jsp?arnumber=01234194>

Chapter 2

Subthreshold MOSFET model


The MOS transistor

Output characteristics @ $V_D = V_G$

 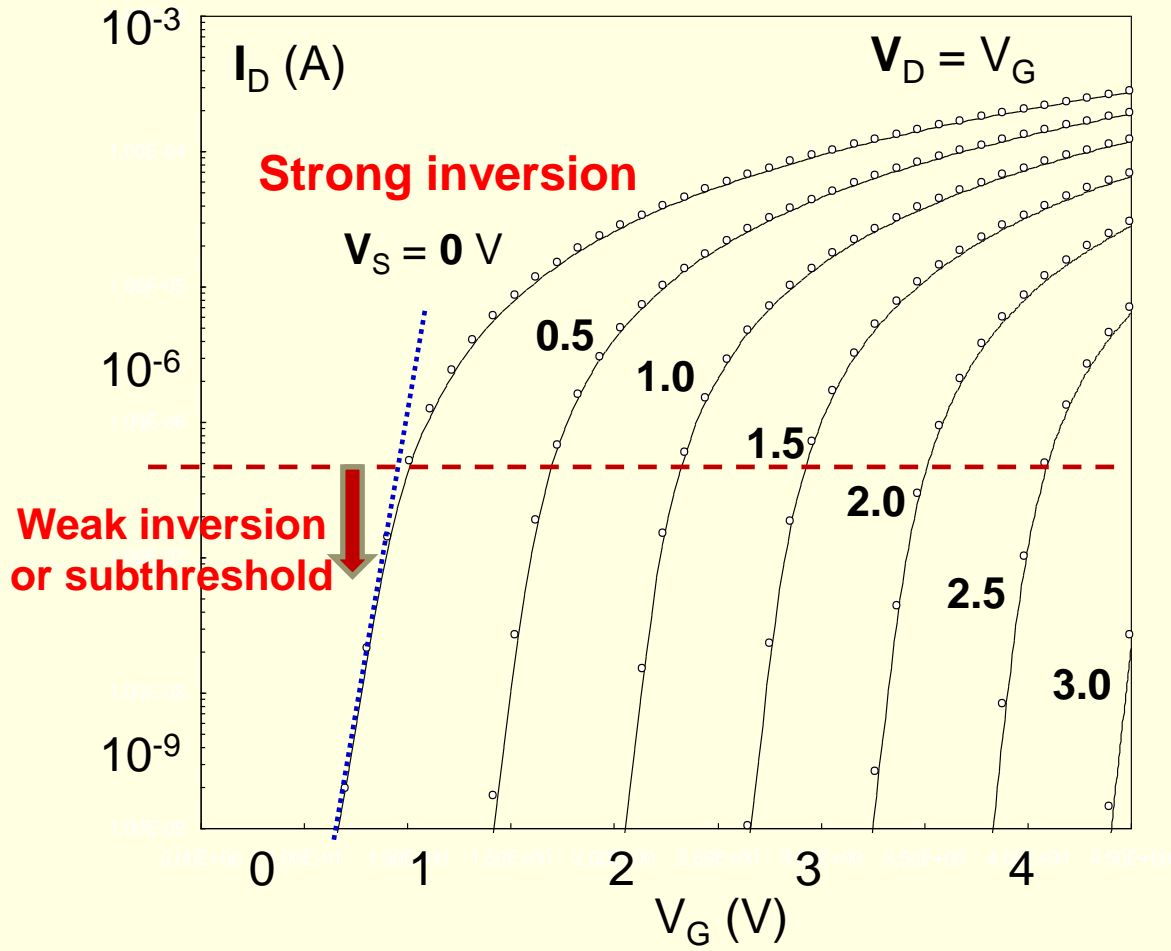

Weak inversion (subthreshold) MOSFET model




Long-channel model

 

$$I_{F(R)} = I_0 e^{\frac{V_G - V_{T0}}{n\phi_t} - \frac{V_{S(D)}}{\phi_t}} \quad I_0 = \mu \frac{W}{L} n C'_{ox} \phi_t^2 e^{-1}$$

$$n = 1 + \frac{C_D}{C_{ox}} \quad \phi_t = \frac{kT}{q} (\approx 26 \text{ mV @ } 300\text{K})$$
   
$$I_D = I_F - I_R = I_0 e^{\left(\frac{V_G - V_{T0} - V_S}{n}\right) / \phi_t} \left[1 - e^{-V_{DS} / \phi_t} \right]$$



Low-frequency small-signal model in weak inversion

Transconductances


$$\Delta I_D = g_{mg} \Delta V_G - g_{ms} \Delta V_S + g_{md} \Delta V_D + g_{mb} \Delta V_B$$

$$g_{mg} - g_{ms} + g_{md} + g_{mb} = 0$$

$$g_{mg} = \frac{\partial I_D}{\partial V_G}, g_{ms} = -\frac{\partial I_D}{\partial V_S},$$

$$g_{md} = \frac{\partial I_D}{\partial V_D}, g_{mb} = \frac{\partial I_D}{\partial V_B}$$
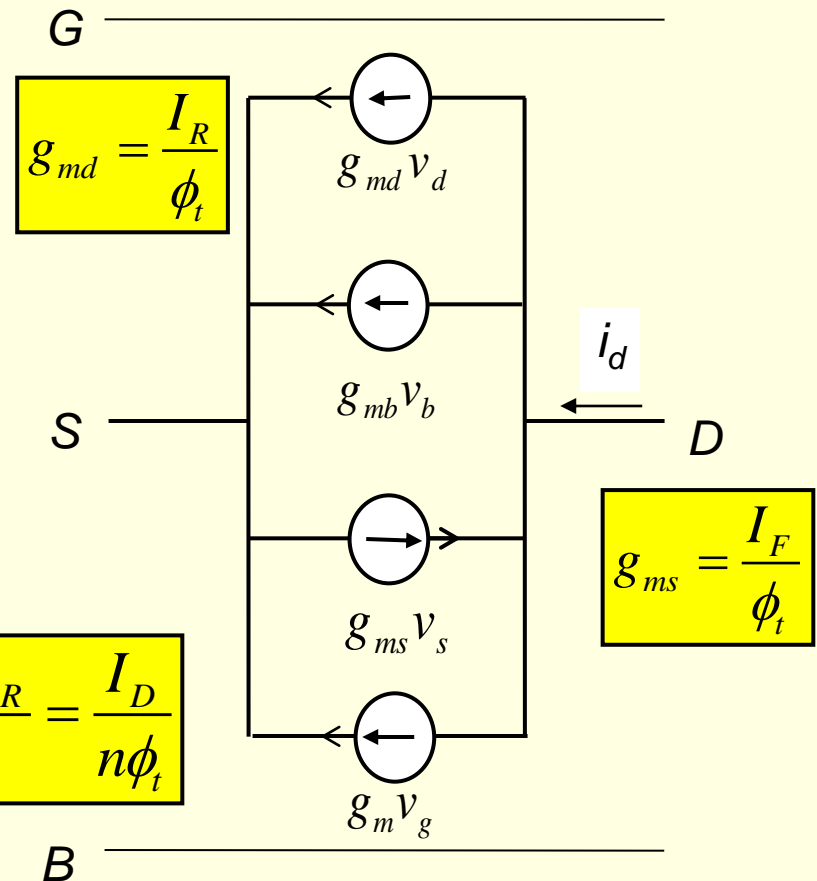
$$g_m = \frac{g_{ms} - g_{md}}{n} = \frac{I_F - I_R}{n\phi_t} = \frac{I_D}{n\phi_t}$$




Low-voltage operation of the common-source amplifier

Intrinsic gain stage

(I_B ideal current source)

weak inversion operation

 


$$|A_V| = \frac{g_m}{g_{md}} = \frac{g_{ms} - g_{md}}{ng_{md}} = \frac{1}{n} \left(\frac{g_{ms}}{g_{md}} - 1 \right)$$


↓

$$\frac{g_{ms}}{g_{md}} = e^{\frac{V_{DS}}{\phi_t}}$$
 
$$g_{ms} = g_{md} \text{ @ } V_{DS} = 0$$



 Low-voltage operation of the common-source amplifier



$$|A_V| = \frac{g_m}{g_{md}} = \frac{g_{ms} - g_{md}}{ng_{md}} = \frac{1}{n} \left(\frac{g_{ms}}{g_{md}} - 1 \right) \quad \frac{g_{ms}}{g_{md}} = e^{\frac{V_{DS}}{\phi_t}}$$

$$|A_V| = \frac{1}{n} \left(e^{\frac{V_{DS}}{\phi_t}} - 1 \right)$$

or




$$V_{DS} = \phi_t \ln(1 + n|A_V|)$$

$$V_{DS} = \phi_t \ln(1 + n|A_V|)$$

$$V_{DS} = \phi_t \ln(2) \quad \text{for } n = |A_V| = 1$$

Low-voltage operation of the CMOS inverter

Minimum supply voltage for amplification $|A_V| = 1$
 'ideal' MOSFET $n = 1$

   

$$V_{DS} = \phi_t \ln(1 + n|A_V|)$$

$$V_{DS} = V_{DD}$$


$$V_{DD\min} = (\ln 2)\phi_t$$

$$V_{DS} = V_{DD} / 2$$

$$V_{DD\min} = 2(\ln 2)\phi_t$$


J. Meindl, IEEE JSSC, 2000

 Low-voltage operation of the common-gate amplifier



$$A_{v, cg} = \frac{v_o}{v_i} = \frac{g_{ms}}{g_{md}} = e^{\frac{qV_{DS}}{kT}}$$


 
The common-gate amplifier provides a voltage gain of greater than unity for $V_{DS} > 0$. → Very useful property for lowering the supply voltage limit for the operation of oscillators (later).



Common-gate Colpitts oscillator

Zero-VT MOSFETs

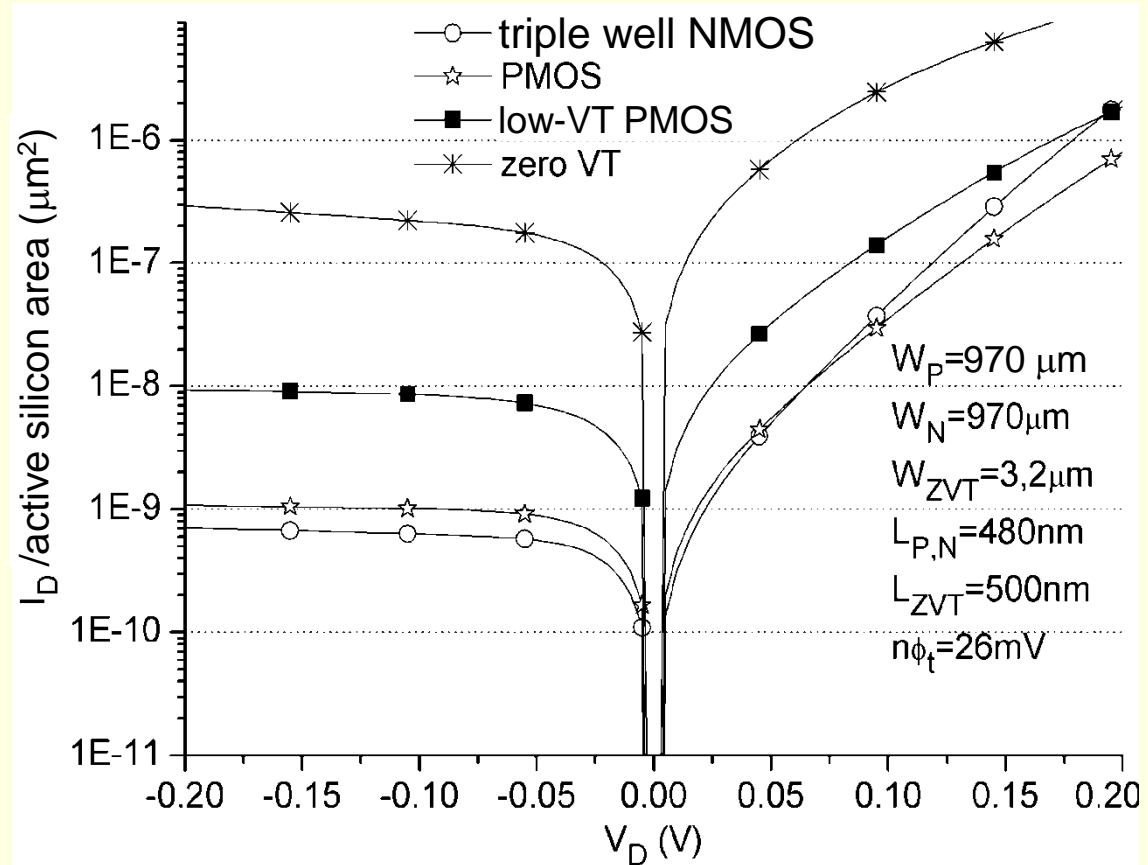 
1 – high current/unit area for low voltages






I-V characteristics of diode-connected MOSFETs (IBM 130nm)

Zero-V_T MOSFETs

2 – high g_m/C (f_T) for low voltages

 

Zero-VT MOSFETs

   

■ $I_D \times V_{DS}$ ($V_S = V_B$) characteristics for a zero-VT transistor with $W/L = 2500\mu\text{m}/420\text{nm}$. For $V_{GS} = 0$ V and $V_{DS} = 25$ mV the values of the common-gate and common-source gains are 1.56 and 0.53, respectively (moderate inversion operation).

References

- R. M. Swanson and J. D. Meindl, “Ion-implanted complementary MOS transistors in low voltage circuits,” *IEEE J. Solid State Circuits*, vol. 7, pp. 146-153, Apr. 1972.
- J. D. Meindl and A. J. Davis, “The fundamental limit on binary switching energy for terascale integration (TSI),” *IEEE J. Solid-State Circuits*, vol. 35, no. 10, pp. 1515-1516, Oct. 2000.
- E. Vittoz, “Weak inversion for ultimate low-power logic”, in *Low-Power Electronics Design*, CRC Press, 2005.
- C. Galup-Montoro and M. C. Schneider, "[Mosfet Modeling For Circuit Analysis And Design](#)", International Series on Advances in Solid State Electronics and Technology, World Scientific, 2007
- Márcio Cherem Schneider and Carlos Galup-Montoro, *CMOS Analog Design Using All-Region MOSFET Modeling*, Cambridge University Press, 2010.


Chapter 3

Subthreshold CMOS logic and Schmitt trigger

Regenerative Property



What's the minimum supply voltage for "correct" operation?

The Regenerative Property


 


A chain of inverters

 
 
Regenerative property: a disturbed signal gradually converges back to V_{OL} or V_{OH} after passing a number of logical stages.



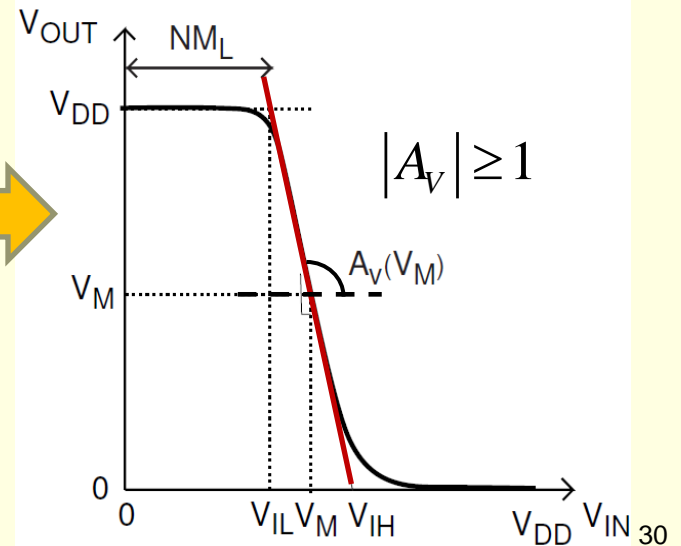 To be regenerative the VTC must present voltage gain greater than 1 in absolute value



THE CMOS INVERTER IN WEAK INVERSION - 1

 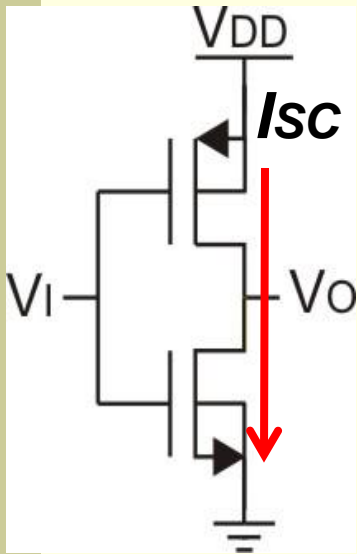

| VDD | VoH (Vi = 0) | VoL (Vi = VDD) |
|--------|----------------|------------------|
| 200 mV | 200 mV | 0mV |
| 50 mV | 46.6 mV | 3.4mV |

Note that:

THE CMOS INVERTER IN WEAK INVERSION - 2

In the ideal case of NMOS and PMOS transistors with the same strength


$$\left| \frac{dV_o}{dV_I} \right|_{V_o = \frac{V_{DD}}{2}} = \frac{e^{\frac{V_{DD}}{2 \cdot \phi_t}} - 1}{n}$$

- The minimum operating supply voltage of the inverter and any CMOS static logic gate must be at least equal to unity, *i.e.*

$$\left| \frac{dV_o}{dV_I} \right|_{V_o = \frac{V_{DD}}{2}} = 1 \qquad \left| \frac{dV_o}{dV_I} \right|_{V_o = \frac{V_{DD}}{2}} = \frac{e^{\frac{V_{DD}}{2 \cdot \phi_t}} - 1}{n}$$

$$V_{DD\min} = 2\phi_t \ln(2) = 36\text{mV at } 300\text{K} \qquad \text{for } n=1$$




6-T Schmitt trigger - 1

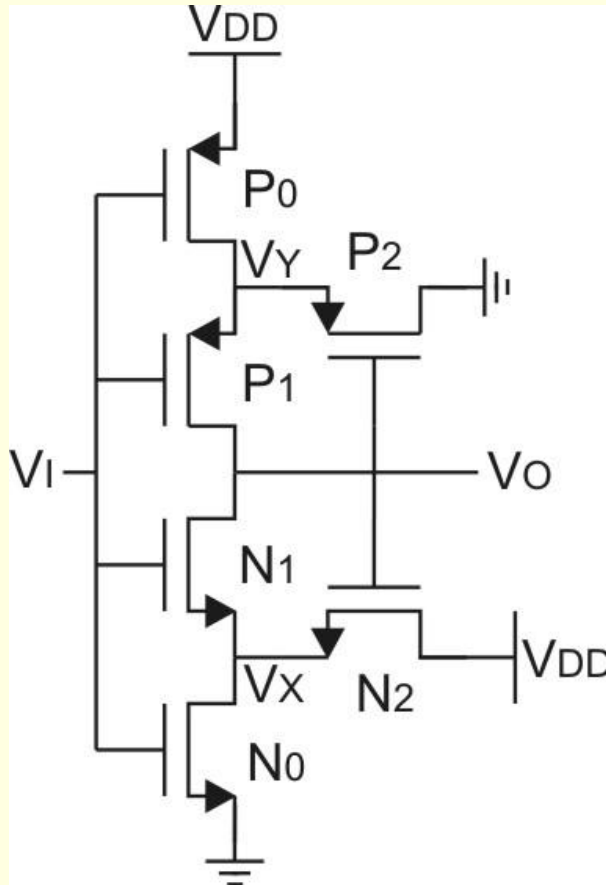

- *2 internal nodes (VX and VY)*
- *Feedback transistors (P2/N2) controlled by the output*
- *Hysteresis dependent on VDD & relative transistor strength*
- *Modeled in strong inversion but not in weak inversion*
 - *For symmetric operation, corresponding NMOS and PMOS MOSFETs have the same current capability.*



6-transistor (6-T) Schmitt Trigger

6-T Schmitt trigger - 2

   

Output characteristics of N and P networks

6-T Schmitt trigger - 3

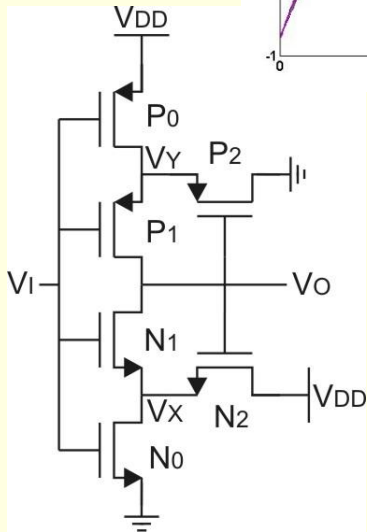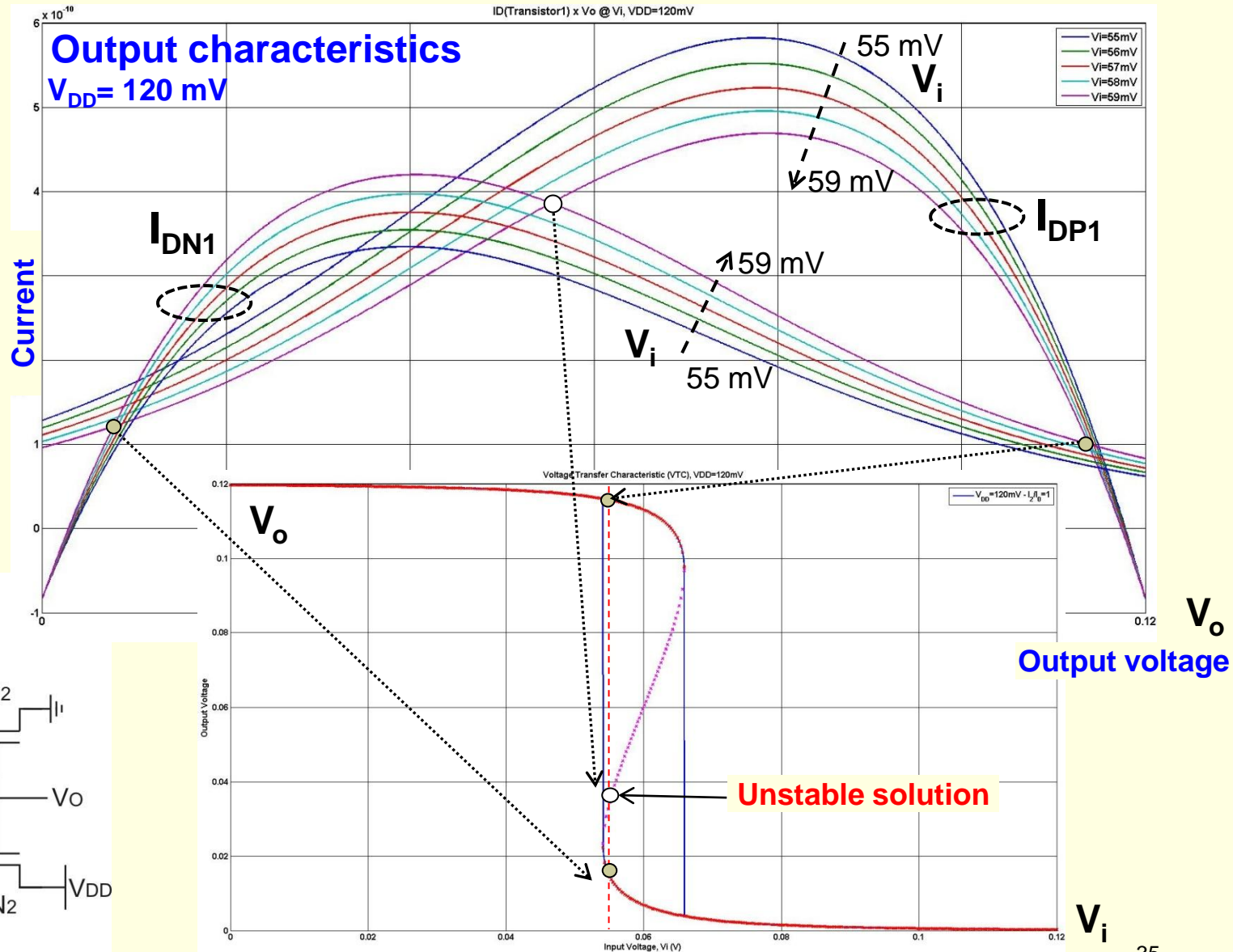


6-T Schmitt trigger - 4

KCL for V_x, V_y, V_o

Symmetric ST $n_N = n_P = 1, V_{TN} = |V_{TP}|,$

$I_{N0} = I_{P0} = I_0, I_{N1} = I_{P1} = I_1, I_{N2} = I_{P2} = I_2$

Loop to solve numerically

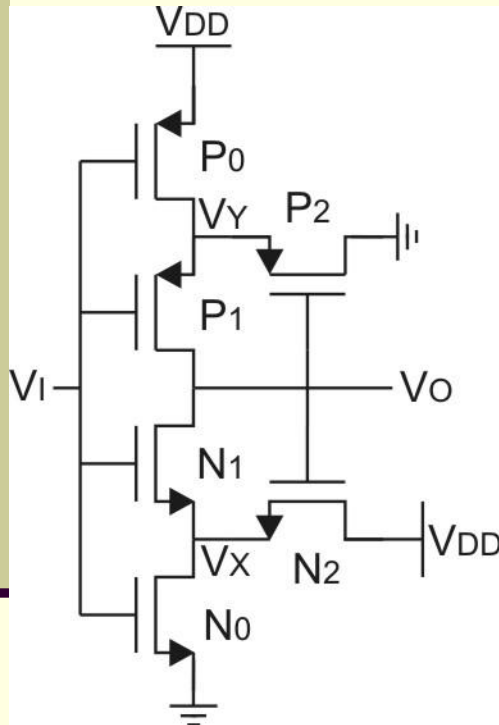

$$e^{\frac{V_Y}{\phi_t}} = \frac{I_0 \cdot e^{\frac{V_{DD}}{\phi_t}} + I_1 \cdot e^{\frac{V_O}{\phi_t}} + I_2 \cdot e^{\frac{V_I - V_O}{\phi_t}}}{I_0 + I_1 + I_2 \cdot e^{\frac{V_I - V_O}{\phi_t}}}$$

$$e^{\frac{V_I - V_X}{\phi_t}} - e^{\frac{V_I - V_O}{\phi_t}} = e^{\frac{V_Y - V_I}{\phi_t}} - e^{\frac{V_O - V_I}{\phi_t}}$$

$$e^{\frac{V_X}{\phi_t}} = \frac{I_0 + I_1 + I_2 \cdot e^{\frac{V_O - V_I}{\phi_t}}}{I_0 + I_1 \cdot e^{\frac{-V_O}{\phi_t}} + I_2 \cdot e^{\frac{V_O - V_I}{\phi_t}} \cdot e^{\frac{-V_{DD}}{\phi_t}}}$$

P-network

$$I_{DP0} = I_{DP1} + I_{DP2}$$

$$I_{DP1} = I_{DN1}$$



N-network

$$I_{DN0} = I_{DN1} + I_{DN2}$$

$$I_{N(P)} = I_{ON(P)} \cdot e^{\frac{-|V_{TN(P)}|}{n_{N(P)} \cdot \phi_t}}$$

6-T Schmitt trigger - 5

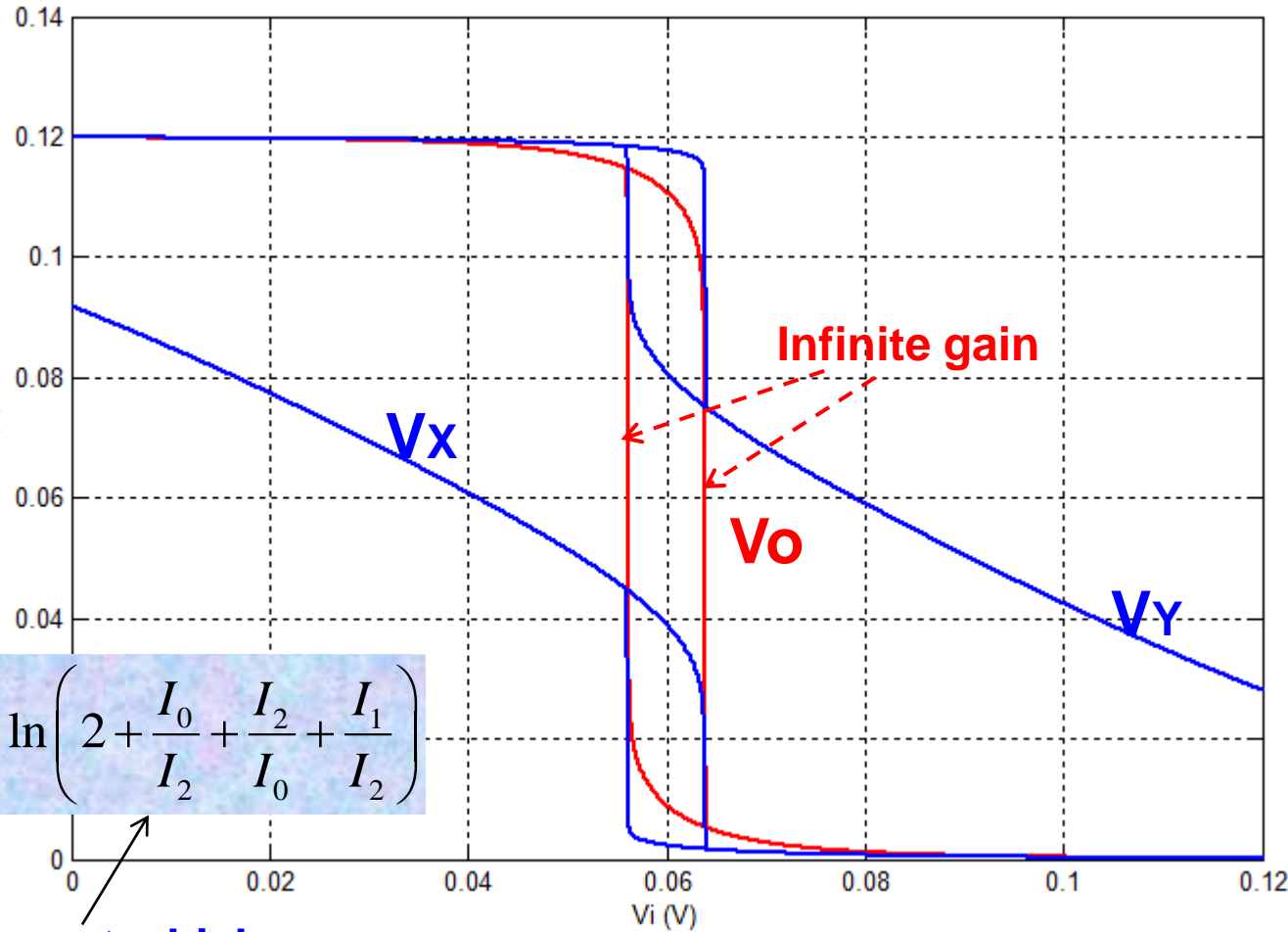
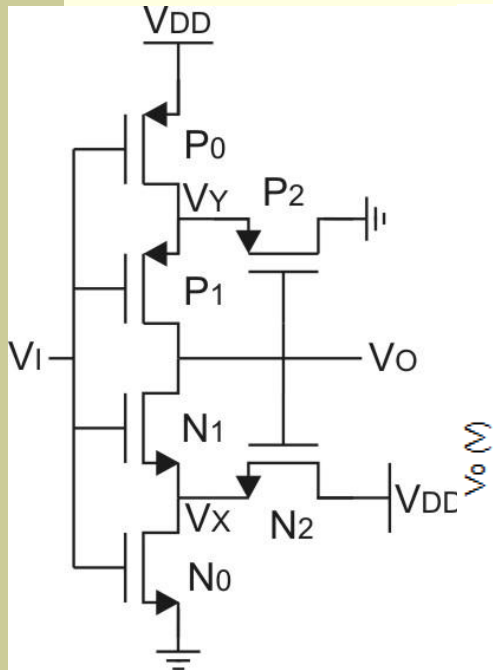
$$I_0 = I_1 = I_2 = 1 \text{ nA}, V_{DD} = 120 \text{ mV}$$



$$V_{DD} > 2\phi_t \ln \left(2 + \frac{I_0}{I_2} + \frac{I_2}{I_0} + \frac{I_1}{I_2} \right)$$

Supply voltage at which hysteresis starts to appear


6-T Schmitt trigger - 6

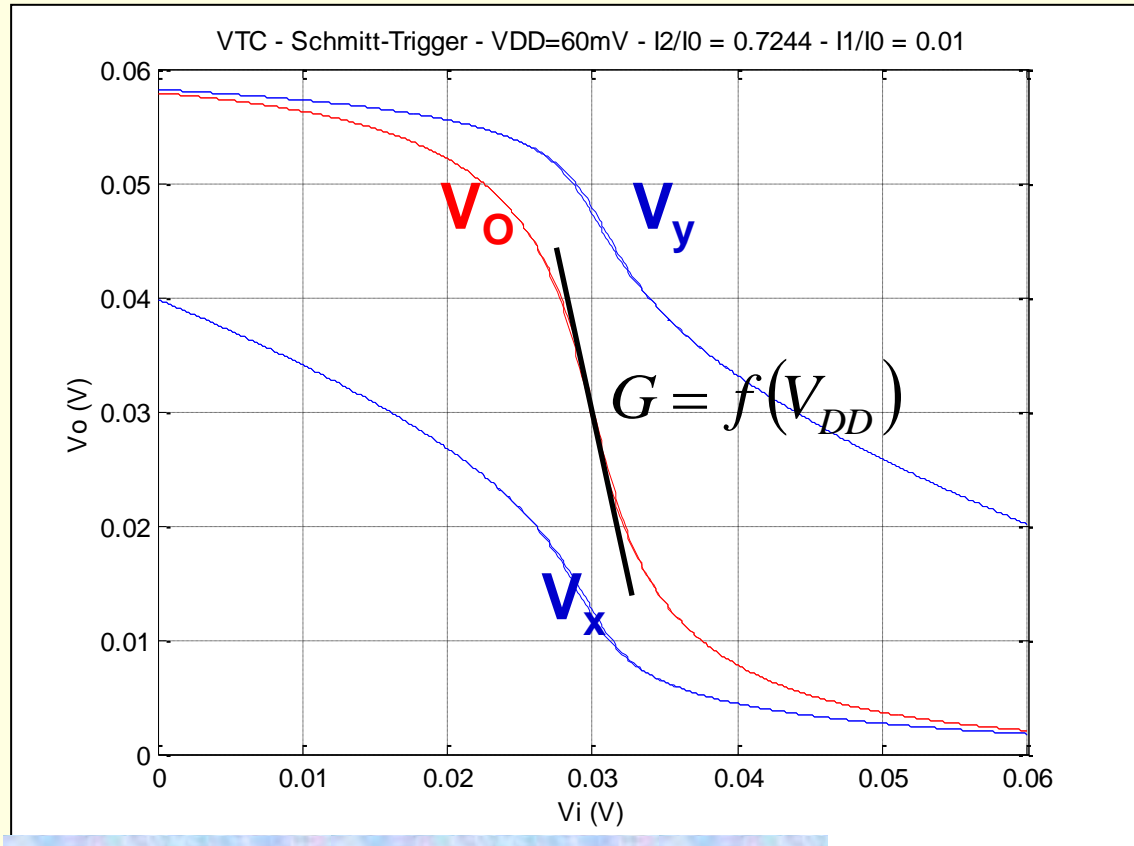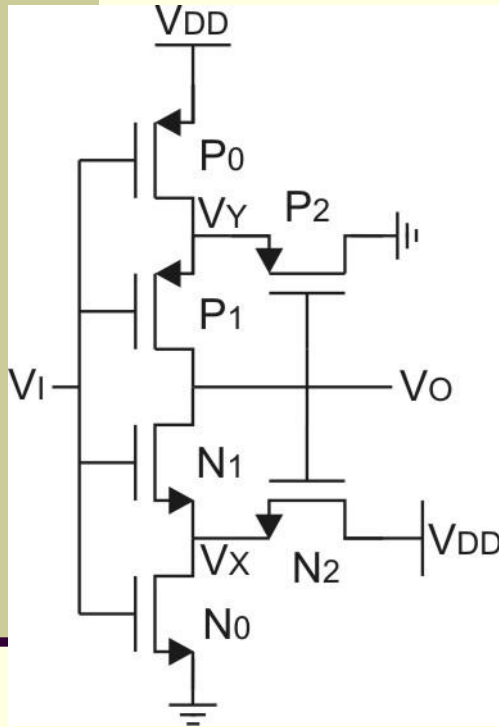

$$V_{DD} < 2\phi_t \ln \left(2 + \frac{I_0}{I_2} + \frac{I_2}{I_0} + \frac{I_1}{I_2} \right)$$

No hysteresis

6-T Schmitt trigger - 7

 

| V_{DD} (mV) | $I_2/I_0 \text{ opt}$ (A/A) | ST Gain | St. Inv. Gain |
|------------------|--------------------------------|------------|------------------|
| 70 | 0.91 | -18.6 | -2.86 |
| 65 | 0.81 | -9.00 | -2.51 |
| 60 | 0.73 | -5.47 | -2.18 |
| 55 | 0.65 | -3.76 | -1.89 |
| 50 | 0.58 | -2.73 | -1.63 |
| 45 | 0.50 | -2.05 | -1.38 |
| 40 | 0.44 | -1.56 | -1.16 |
| 35 | 0.39 | -1.20 | -0.97 |
| 31.5 | 0.33 | -1.00 | -0.84 |


$$\left. \frac{I_1}{I_0} \right|_{\text{OPTIMUM}} = 0$$

$$\left. \frac{I_2}{I_0} \right|_{\text{OPTIMUM}} = \frac{\sqrt{1 + e^{\frac{V_{DD}}{2\phi_t}} - e^{-\frac{V_{DD}}{2\phi_t}} - 1}}{1 + e^{-\frac{V_{DD}}{2\phi_t}}}$$

**Strength ratios for
highest gain for a
given V_{DD}**

6-T Schmitt trigger - 8

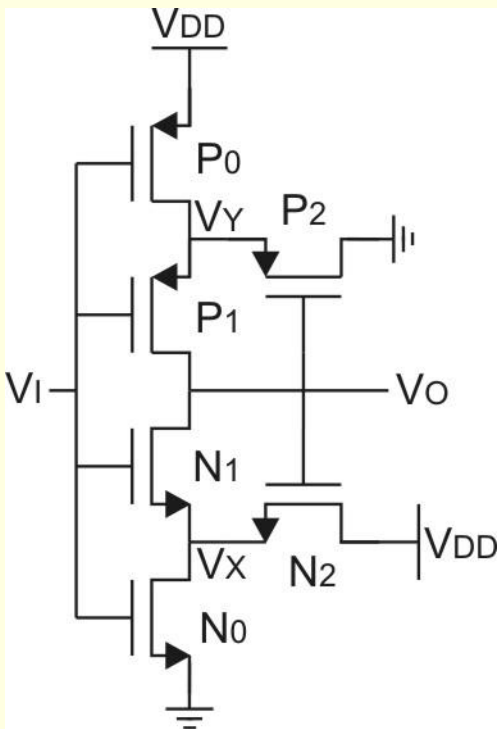What is the minimum operating voltage that results in gain = -1 ?




$$V_{DD\min} = 2\phi_t \ln\left(\frac{1}{\sqrt{73}-8}\right) = 31.5\text{mV at } 300\text{K}$$



73 is the best number !


6-T Schmitt trigger - 9

 ST inverter is less sensitive to process parameter (V_T) spreading than the standard inverter.




6-T Schmitt trigger - 10

NOR gate

 


ST-NOR gate

 


TEST CHIP

 $VTC - ST \times INV - V_{DD} = 150, 100, 75, 50 \text{ mV}$



IBM 180nm
CMRF7 - MOSIS

 

$I_1/I_0 = 0.1$
 $I_2/I_0 = 0.4$

References


- J. D. Meindl and A. J. Davis, “The fundamental limit on binary switching energy for terascale integration (TSI),” *IEEE J. Solid-State Circuits*, vol. 35, no. 10, pp. 1515-1516, Oct. 2000.
- E. Vittoz, “Weak inversion for ultimate low-power logic”, in *Low-Power Electronics Design*, CRC Press, 2005.
- J. Rabaey, *Low Power Design Essentials*, Springer, New York, NY, 2009.
- N. Lotze and Y. Manoli, “A 62mV 0.13um CMOS standard-cell-based design technique using Schmitt-Trigger logic”, *IEEE Journal of Solid-State Circuits*, vol. 47, no. 1, pp 47-60, Jan 2012.

Chapter 4


ULV rectifiers

Ultra-low-voltage diode circuits

 Dickson analysis of voltage multipliers: constant threshold voltage diode model, **not appropriate for low voltage operation**



$$V_L = V_P - V_{ON}$$

 

How to substitute the constant 'diode voltage drop' model?
Use the i-v characteristic of the diode and the load current


$$I_D = I_S \left[e^{\frac{V_D}{n\phi_t}} - 1 \right]$$

$$\phi_t = \frac{kT}{q}$$

$$n \sim 1 \text{ to } 1.5$$

Voltage rectifier with pure capacitive load

 Steady-state analysis Assumption: very low ripple (high C)
 → $V_o \cong \text{constant}$



$$\frac{1}{T} \int_{-T/2}^{T/2} I_D dt = \frac{I_S}{T} \int_{-T/2}^{T/2} [e^{\frac{V_D}{n\phi_t}} - 1] dt = \frac{I_S}{T} \left[\int_{-T/2}^0 \left(e^{\left(\frac{-V_P - V_o}{n\phi_t} \right)} - 1 \right) dt + \int_0^{T/2} \left(e^{\left(\frac{V_P - V_o}{n\phi_t} \right)} - 1 \right) dt \right] = 0$$

$$\frac{V_o}{n\phi_t} = \ln \left[\frac{e^{V_P/n\phi_t} + e^{-V_P/n\phi_t}}{2} \right] = \ln \left[\cosh(V_P/n\phi_t) \right]$$

$$V_P \gg n\phi_t$$

Power Detector


$$V_P \ll n\phi_t \rightarrow \frac{V_o}{n\phi_t} \cong \frac{1}{2} \left(\frac{V_P}{n\phi_t} \right)^2$$

Peak Detector


$$V_P \gg n\phi_t \rightarrow V_L \cong V_P - n\phi_t \ln 2$$

**Diode "ON"
voltage drop**

Input

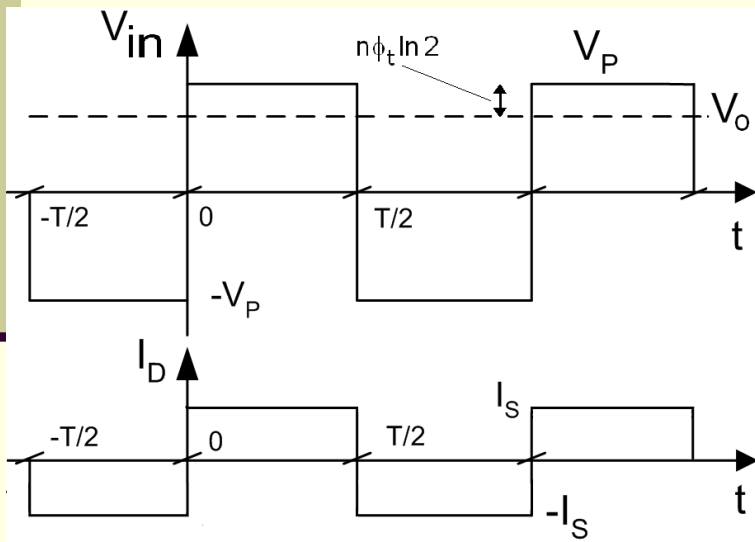

Voltage rectifier with DC load - 1

 



$$\frac{1}{T} \int_{-T/2}^{T/2} I_D dt = \frac{I_S}{T} \left[\int_{-T/2}^0 \left(e^{\left(\frac{-V_P - V_o}{n\phi_t} \right)} - 1 \right) dt + \int_0^{T/2} \left(e^{\left(\frac{V_P - V_o}{n\phi_t} \right)} - 1 \right) dt \right] = I_L$$

Diode "ON"
voltage drop

$$\frac{V_o}{n\phi_t} = \ln \left[\frac{\cosh(V_P / n\phi_t)}{1 + I_L / I_S} \right]$$



Waveforms for
 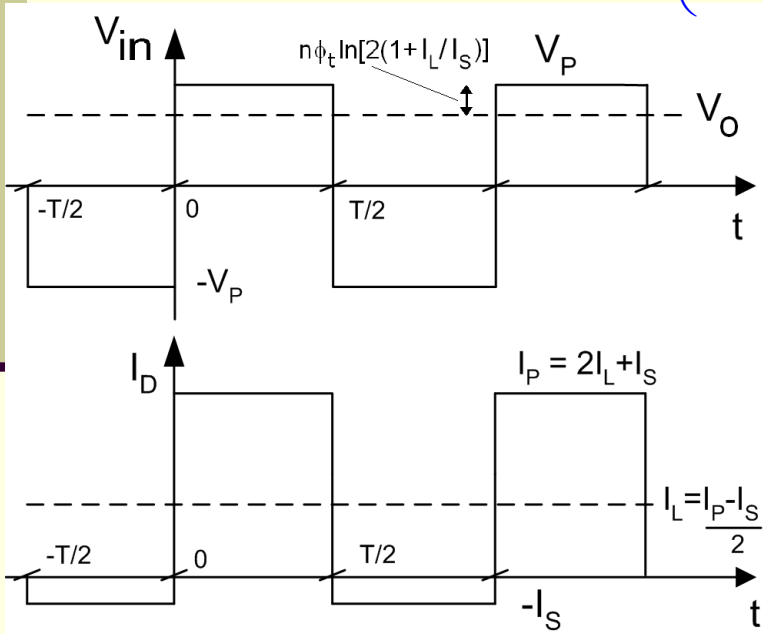
$$V_P > n\phi_t \Rightarrow V_o \cong V_P - n\phi_t \ln \left(\frac{I_P + I_S}{I_S} \right)$$



Voltage rectifier with DC load - 2

Output voltage ripple

  

The discharge rate of the capacitor



$$I_C = \frac{dQ_C}{dt} = C \frac{dV_C}{dt} \approx I_L + I_S$$

$$\int_{-T/2}^0 dV_C = \Delta V \approx \frac{I_L + I_S}{C} \frac{T}{2} = \frac{I_L + I_S}{2fC}$$

The voltage multiplier - 1


N-stage voltage multiplier

Voltage doubler

  

- Generation of voltages higher than V_{DD} for EEPROMs, flash memories.
- Energy harvesting for RFID tag chips


The voltage multiplier - 2

 

Output voltage

$$\frac{V_L}{n\phi_t} = N \ln \left[\frac{I_0(V_A/n\phi_t)}{1 + I_L/I_S} \right]$$

 Modified Bessel function,
first kind, order zero



Power conversion efficiency

$$PCE = \frac{P_{load}}{P_{in}} = \frac{V_L I_L}{P_{load} + P_{loss}}$$


PCE is
maximized for

$$\frac{I_L}{I_S} = \frac{V_L}{Nn\phi_t}$$



The voltage multiplier - 2

Model of the N-stage voltage multiplier

 
$$k_c = \frac{R_{ant} V_L I_L}{(n\phi_t)^2}$$



  
Design for minimum available power/maximum range in terms of k_c



What about diodes?

 




 
- Low (zero)-VT
- Standard-VT
- pn junction



Diode-connected zero-VT MOSFET
- high drive capability

AC/DC converter in 130 nm CMOS technology

24-stage rectifier

    

Matching network



References

- A. Jair Cardoso, M. C. Schneider, C. Galup-Montoro; "Design of very low voltage CMOS rectifier circuits"; *IEEE Circuits and Systems for Medical and Environmental Applications Workshop (CASME 2010)*, Mérida, Mexico, Dec. 2010.
- Adilson Jair Cardoso *et al.* "Teaching low voltage electronics: the case of the rectifier circuit", *IEEE International Conference on Microelectronic Systems Education (MSE)*, San Diego, June 2011.
- A. J. Cardoso *et al.* , "Analysis of the rectifier circuit valid down to its low-voltage limit" , *IEEE Transactions on Circuits and Systems I: Regular Papers*, Jan. 2012.
- C. Galup-Montoro, M. C. Schneider, and M. B. Machado, "Ultra-low-voltage operation of CMOS analog circuits: amplifiers, oscillators, and rectifiers," *IEEE Trans. on Circuits and Syst. II, Exp. Briefs*, vol. 59. No.12, pp. 932-36, Dec. 2012.
- L . G. de Carli *et al.* , "Maximizing the Power Conversion Efficiency of Ultra-Low-Voltage CMOS Multi-Stage Rectifiers," *IEEE Transactions on Circuits and Systems I: Regular Papers*, April 2015.


Chapter 5

ULV oscillators and applications

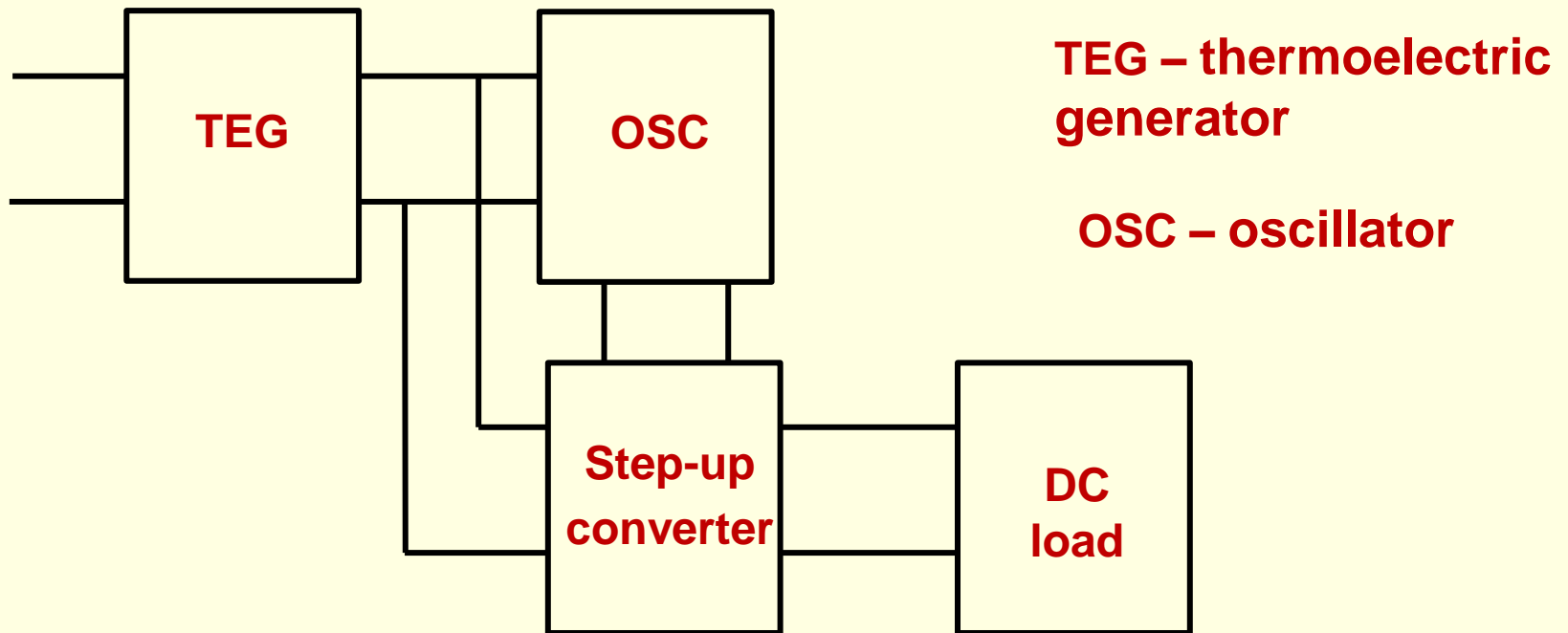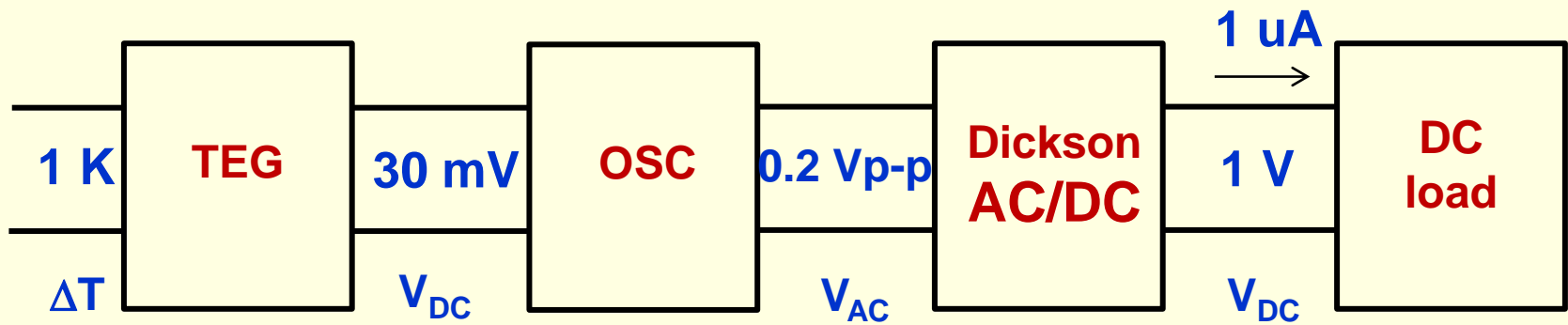
Application of ULV oscillators for energy harvesters



 Inductive ring (X-coupled) oscillator - 1



Cross-coupled LC oscillator

 

$$\frac{V_{out}}{V_{in}} = - \frac{g_m}{g_{md} + G_P} \frac{1}{1 - j \tan \phi} = -1$$

$$\tan \phi = \frac{1 - LC\omega^2}{\omega L(g_{md} + G_P)}$$

Criterion for oscillation (Barkhausen)


$$\phi = 0 \quad \& \quad V_{out}/V_{in} = -1$$

$$\frac{g_m}{g_{md} + G_P} = 1$$

$$\omega^2 LC = 1$$

What's the minimum V_{DD} for oscillation?

Inductive ring oscillator - 2

 

Cross-coupled LC oscillator

Oscillation frequency $\omega^2 LC = 1$

Voltage gain $\frac{g_m}{g_{md} + G_P} = 1$

What's the minimum V_{DD} for oscillation?

Recall that $g_m = \frac{g_{ms} - g_{md}}{n}$


Voltage gain=1 \Rightarrow (i) $\frac{g_{ms}}{g_{md}} = 1 + n \left(1 + \frac{G_P}{g_{md}} \right)$

In weak inversion \Rightarrow (ii) $\frac{g_{ms}}{g_{md}} = e^{V_{DS}/\phi_t} = e^{V_{DD}/\phi_t}$ since $V_G = V_D = V_{DD}$

$$V_{DD,\min} = \phi_t \ln \left[1 + n \left(1 + \frac{G_P}{g_{md}} \right) \right] = \phi_t \ln [1 + n] \quad \text{for } \frac{G_P}{g_{md}} \ll 1$$

Similar to the result (/2) of the CMOS inverter

Inductive ring oscillator - 3

 



Questions:

1. How to reduce $V_{DD,min}$?
2. How to increase the V_{DD} -limited voltage swing?

Introduce voltage gain from drain to gate

Change topology, e. g., take advantage of CG gain



Enhanced swing IRO (ESRO)

 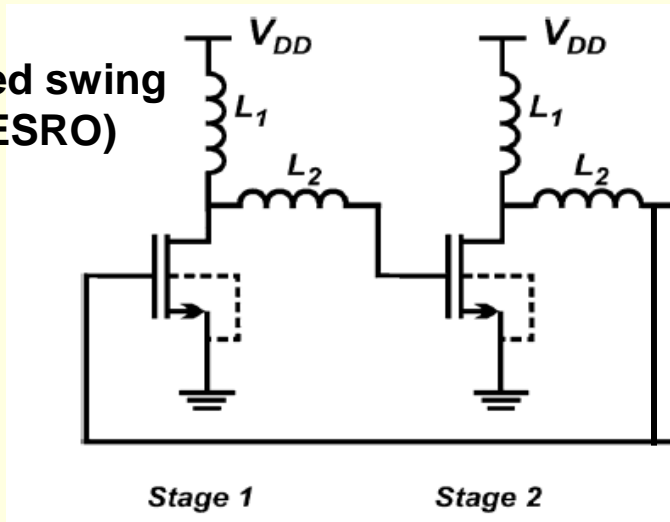

Enhanced swing Colpitts oscillator (ESCO) *

* T. W. Brown et al, *IEEE JSSC*, Aug. 2011.

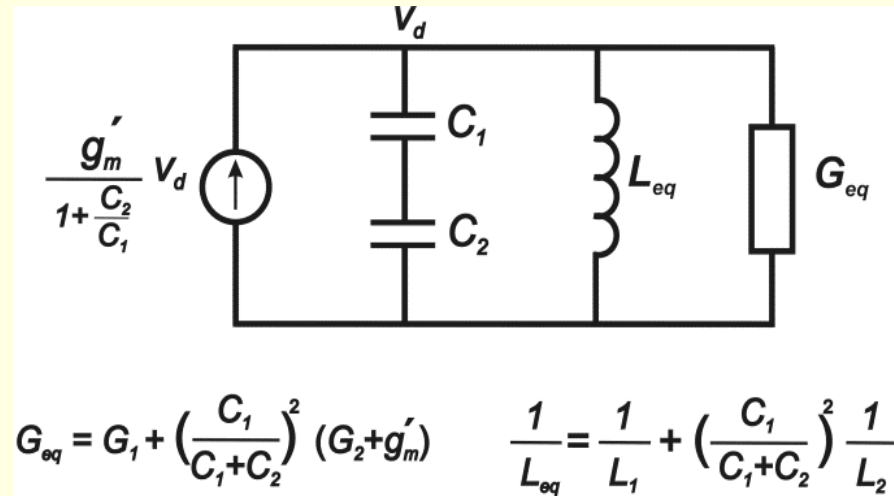 The enhanced-swing Colpitts oscillator (ESCO)



$$v_s \cong \frac{v_d}{1 + \frac{C_2}{C_1}} \rightarrow g_{ms} v_s - g_{md} v_d \cong g'_m v_s \quad g'_m = g_{ms} - \left(1 + \frac{C_2}{C_1}\right) g_{md}$$



For lossless inductors and capacitors

Weak inversion

$$V_{DDlim} = \frac{kT}{q} \ln \left(1 + \frac{C_2}{C_1} \right)$$

Colpitts oscillator: first prototype


Off-the-shelf components

  

$V_{DD}=22.2 \text{ mV}$

thermoelectric generator

 
24 // NMOS
Zero-VT (ALD 1108)
 $V_T=59 \text{ mV}$, $I_S=11.2 \text{ }\mu\text{A}$



Colpitts oscillator: second prototype

Zero-VT
IBM 130 nm


L2

 



L1

C1



W/L = 2500 μm / 0.42 μm

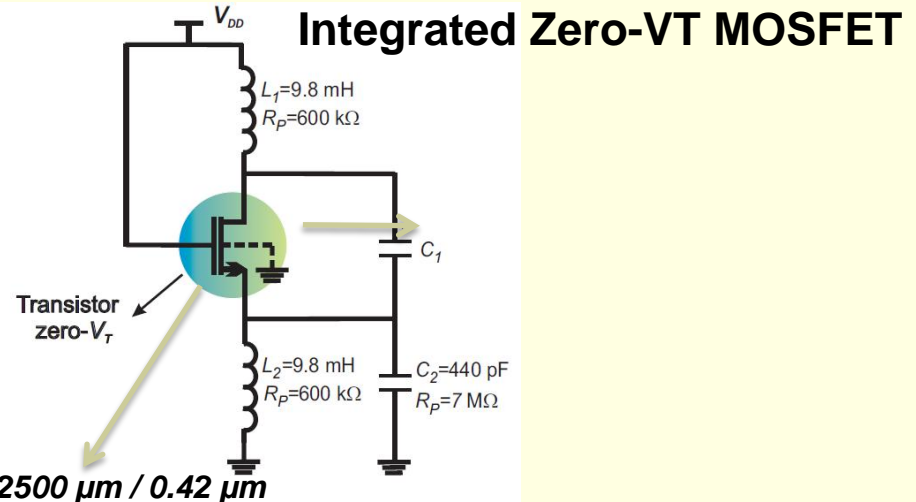


$V_{PP} \approx 440\text{ mV}$

  

Colpitts oscillator – IC prototype

 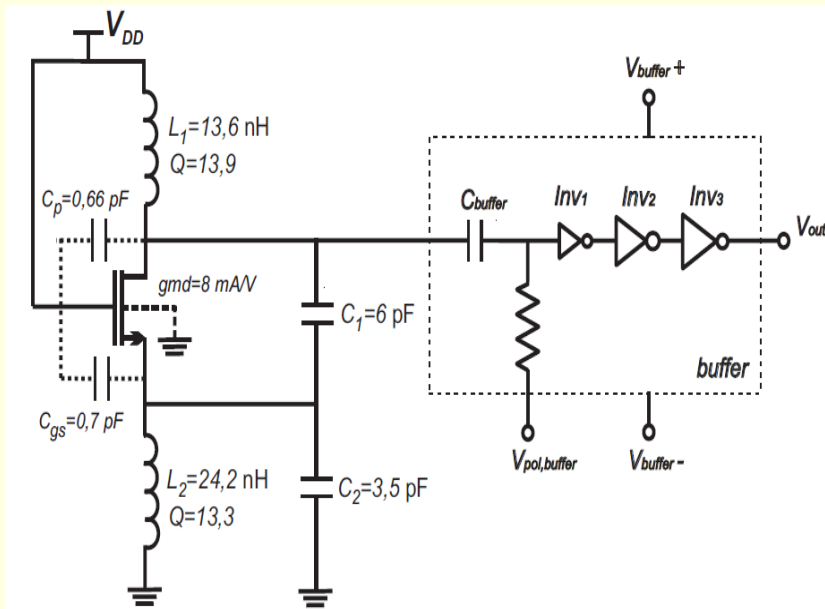

130 nm technology

 

Enhanced-swing ring oscillator (ESRO)

 
 


Fig. 12. Simulated (dotted line) and experimental (solid line) peak-to-peak gate voltage versus supply voltage of the ES inductive-load ring oscillator.

 
 


TABLE I
EXPERIMENTAL RESULTS FOR THE OSCILLATION FREQUENCY AND MINIMUM SUPPLY VOLTAGE OF THE OSCILLATOR TOPOLOGIES

| Topology | Theoretical $V_{dd} \text{ (min) }^*$ | IC prototype 130nm CMOS | | Discrete prototype | |
|----------|--|-------------------------|-----------|------------------------|-----------|
| | | $V_{dd} \text{ (min)}$ | f_{osc} | $V_{dd} \text{ (min)}$ | f_{osc} |
| ILRO | $\phi_t \ln(1+n)$ | 53 mV | 550 MHz | 50 mV | 11 MHz |
| ESRO | $\phi_t \ln\left(1+n\frac{L_1}{L_1+L_2}\right)$ | 32 mV | 400 MHz | 3.5 mV | 1.1 MHz |
| ESCO | $\phi_t \ln\left(1+\frac{C_2/C_1}{1+L_1/L_2}\right)$ | 86 mV | 700 MHz | 15 mV | 108 kHz |

* For lossless passive devices and operation of MOSFETs in weak inversion

Values of components:

ILRO – IC prototype – $L = 100 \text{ nH}$, $Q = 8$.

ILRO – discrete prototype – $L = 4.6 \text{ uH}$, $Q = 50$.




ESRO – IC prototype – $L_1 = 20 \text{ nH}$, $Q_1 = 9$; $L_2 = 80 \text{ nH}$, $Q_2 = 8$.

ESRO – discrete prototype – $L_1 = 4.6 \text{ uH}$, $Q_1 = 55$, $L_2 = 1.2 \text{ mH}$, $Q_2 = 60$.

ESCO – IC prototype – $L_1 = 13.6 \text{ nH}$, $Q_1 = 13.9$, $L_2 = 24.2 \text{ nH}$, $Q_2 = 13.3$, $C_1 = 6 \text{ pF}$, $C_2 = 3.5 \text{ pF}$.

ESCO – discrete prototype – $L_1 = L_2 = 9.8 \text{ mH}$, $Q_1 = Q_2 = 80$, $C_1 = 1.54 \text{ nF}$, $C_2 = 0.44 \text{ nF}$.

Energy harvester

 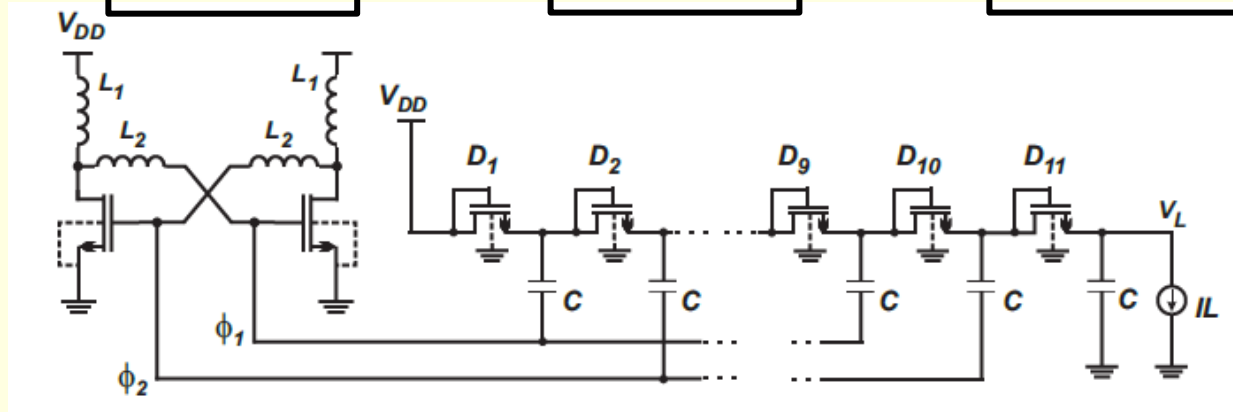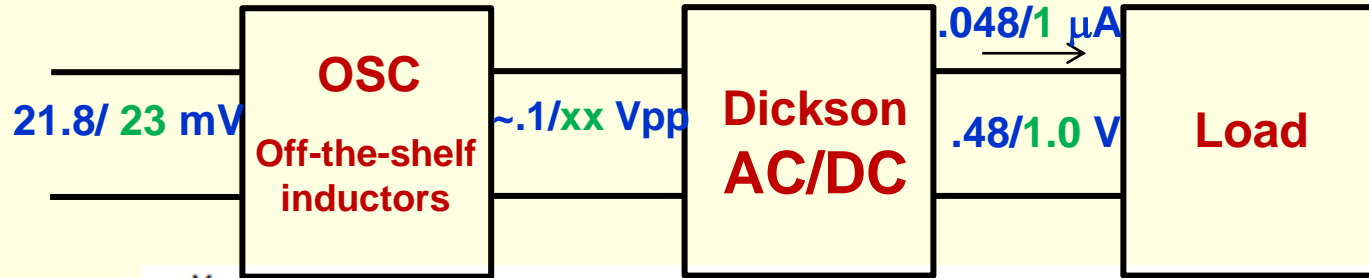

References

- C. Galup-Montoro, M. C. Schneider and M. B. Machado; "On the minimum supply voltage for CMOS analog circuits: rectifiers and oscillators", MOS Modeling and Parameter Extraction Working Group MOS-AK/GSA Workshop Dec. 7, 2011 Washington DC.
- C. Galup-Montoro, M. C. Schneider, and M. B. Machado, "Ultra-low-voltage operation of CMOS analog circuits: amplifiers, oscillators, and rectifiers," *IEEE Trans. on Circuits and Syst. II, Exp. Briefs*, Dec. 2012.
- M. B. Machado *et al.* , "On the minimum supply voltage for MOSFET oscillators", *IEEE Transactions on Circuits and Systems I: Regular Papers*, Feb 2014.
- M. B. Machado *et al.*, "Fully integrated inductive ring oscillators operating at VDD below $2kT/q$," *Analog Integrated Circuits and Signal Processing*, Jan 2015.